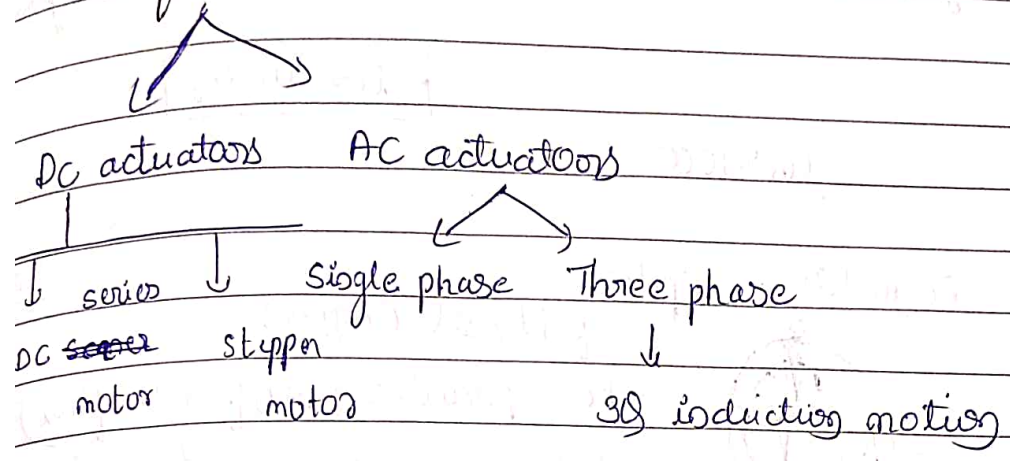


Actuators :


Actuator is device which initiates an action.
 action (movement)

classification



DC motor :->

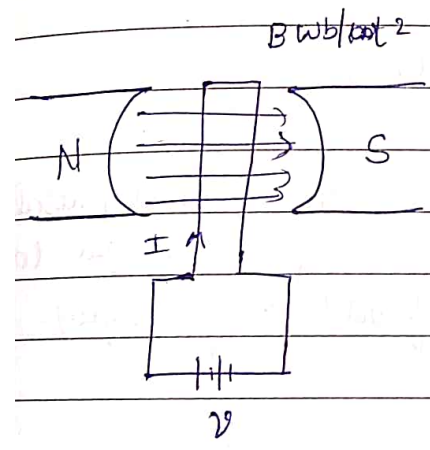input - DC electrical input
 output - mechanical force




Principle : current carrying conductor lying in a magnetic field experiences force.

$$F = BIL \sin \theta$$

The direction of force follows left hand rule

Construction : DC motor has two parts

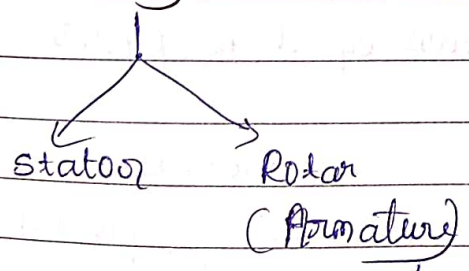

- ① Stator → stationary
- ② Rotor → moving

↓ in DC motor Rotor is called armature


★ Stator:

part which provides magnetic flux


high silicon content steel - permeability is high

$$\mu = \mu_0 \mu_r$$

$$\mu_r > 1000$$

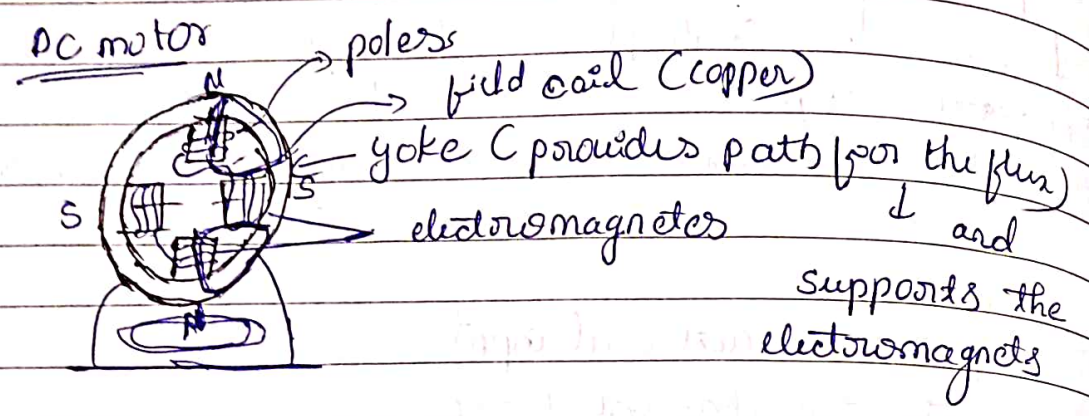

★ Rotor (armature)

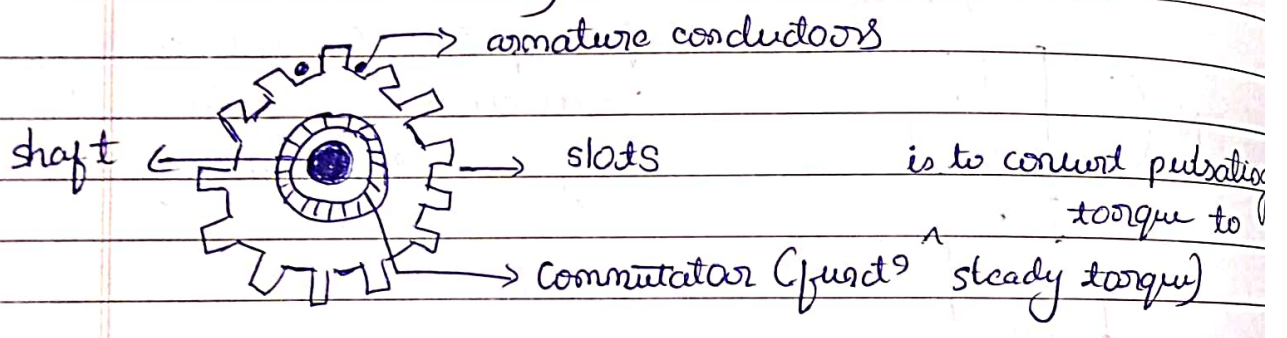

Working of dc motor

2 types of armature winding:


1) LAP \Rightarrow no of parallel paths equal no of poles

2) WAVE \Rightarrow

poles $P = 4$

conductors $Z = 240$

parallel paths $A = 4$

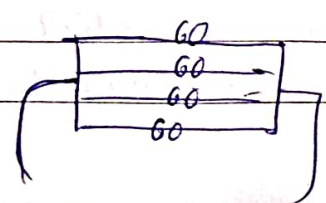

Equivalent circuit of a dc shunt motor:

If the field winding is connected in parallel with the armature winding, then it is a dc shunt motor.

E_b - back emf

V - dc supply voltage

R_a - armature equivalent resistance which is around 1Ω

R_f - field resistance (Conestat) around 100Ω


I_L - line current

I_a - armature current

I_f - field current

* field winding and armature winding are connected in parallel

* R_c is in series with armature

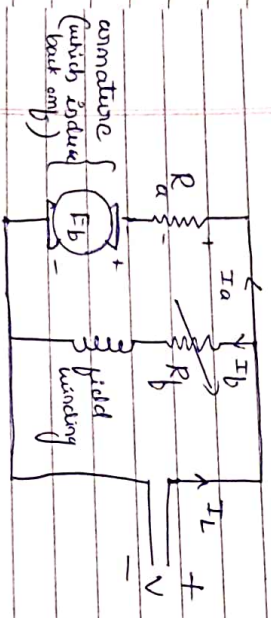

KCL

$$I_L = I_a + I_f$$

KVL

$$V = I_a R_a + E_b$$

$$I_f = \frac{V}{R_f}$$

* In dc shunt motor pole flux remains constant

$$E_b = \frac{P \phi Z N}{60 A} \rightarrow \text{always } \phi \text{ is constant}$$


$$N \propto \frac{1}{\phi} \quad \text{because } \phi \text{ is constant}$$

$$T = 0.159 \phi Z I_a \text{ p/n}$$

* dc shunt motor used in constant speed applications

Equivalent circuit of a dc series motor

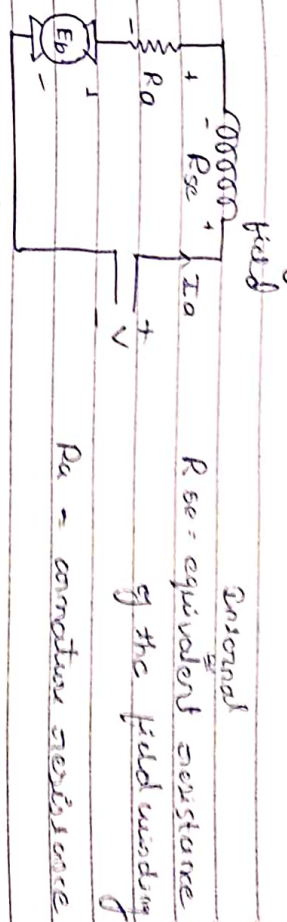If the field winding is connected in series with armature winding, then it is a dc series motor



KVL:

$$V = I_a R_{se} + I_a R_a + E_b$$

$$V = I_a (R_{se} + R_a) + E_b$$

KCL

$$I_L = I_a = I_f = I$$


* when load changes, current changes so flux is not constant

* in dc series motor flux not constant

* The dc series motor is always started with sufficient load applied, since $N \propto \frac{1}{\phi}$ if less load is applied then ϕ is also very small, which results in dangerously high speed, which causes damage to motor & injury to people

hence these motor are used where full load is supplied & then motor start.

DC shunt motor

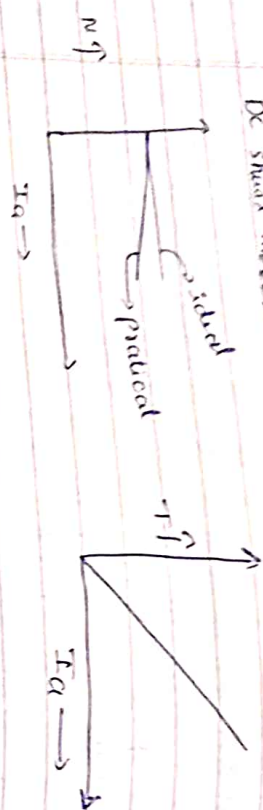

Starting torque is very less


DC series motor

$$I_a \propto \phi$$

$$\phi \propto \frac{1}{N}$$

$$T \propto \phi I_a$$
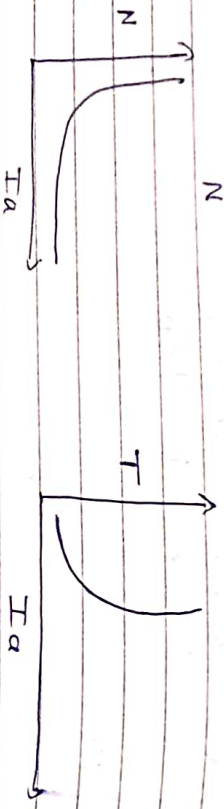
$$T \propto I_a I_a \rightarrow T \propto I_a^2$$



* used for lifting applications

- 1) lift 2) cranes 3) electric traction 4) hoists

Q1) a 6 pole lap wound dc shunt motor has 500 conductors in armature, the R_a is 0.05Ω

Resistance of shunt field is 25Ω find the speed of the motor when it takes $120 A$ from $100 V$ dc supply

→

$$P = 6 \quad Z = 500 \quad R_a = 0.05$$

$$R_f = 25 \Omega \quad N = ? \quad \phi = 0.0001$$

$$I_L = 120 A \quad V = 100$$

$$100 = \frac{E_b + I_a R_a + E_b}{0.0001}$$

$$N = \frac{1}{0.0001}$$

$$E_L = I_a + I_b$$

$$I_L = I_a + I_b$$

$$I_a = 116 A$$

$$V = I_a R_a + E_b$$

$$100 = 116 \times 0.05 + E_b$$

$$E_b = 94.2 V$$

$$E_b = \frac{6 \times 30 \times 10^{-3} \times 500 \times N}{60 \times 6}$$

$$N = 506 \times 10^{-4} \text{ rpm}$$

calculate speed when load by motor is reduced by 25%

load reduced by 25%

$$I_L = 120 \times 0.2 = 24$$

$$120 - 24 = 96 A$$

$$N = \frac{96 \times 10^{-3} \times 500}{0.0001}$$

$$I_L = I_a + I_f$$

$$96 = I_a + 100$$

$$I_a = -4 A$$

$$V = 92 \times 0.05 + E_b$$

$$E_b = 100.5 V$$

$$N = 572.4 \text{ rpm}$$

iii)

$$50\% \text{ of load } T_a = 56 \text{ N}$$

$$T_L = 60 \text{ N}$$

$$N = 553.8 \text{ rpm}$$

iv) 85% of 120 N

$$T_a = 30 \text{ N}$$

$$= 26 \text{ N}$$


$$E_b = 100 - 26 \times 0.05$$

$$= 98.7 \text{ volts}$$

$$N = \frac{E_b \times 60}{\phi Z \pi}$$

$$= \frac{98.7 \times 60}{20 \times 10^{-3} \times 500}$$

$$N = 592.2 \text{ rpm}$$

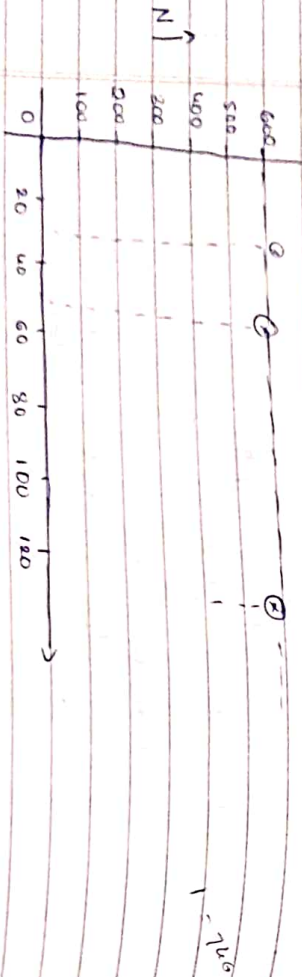

8)

230 V motor has an armature circuit resistance of 0.6Ω . If full load armature current 30 A of the load armature current is 21 A . Find the change in back emf. % change in E_b from no load to full load

→

DC shunt motor C because its speed decreases of T_a possible in shunt motor

$$T_a \text{ FL} = 30 \text{ N}$$

$$T_a \text{ no load} = 1 \text{ N}$$

$$V = 230 \text{ V}$$

$$R_a = 0.6 \Omega$$

$$V = I_a R_a + E_b$$

$$E_b = V - I_a R_a$$

$$= 230 -$$

$$E_{b \text{ FL}} = 212 \text{ V}$$

$$E_{b \text{ NL}} = 230 - 4 \times 0.6$$

$$= 227.6 \text{ V}$$

$$\% \text{ change } E_b = \frac{227.6 - 212}{212} \times 100 = 6.85\%$$

8)

440 V dc shunt motor has an armature resistance of 0.8Ω and field resistance of 200Ω . determine back emf when giving an output of 7.46 kW at 85% efficiency

→

$$V = 440 \text{ V} \quad R_a = 0.8 \Omega$$

$$R_f = 200 \Omega \quad E_b = ?$$

$$1 \text{ hp} = 746 \text{ W}$$

$$\text{Efficiency} = \frac{\text{output}}{\text{input}}$$

$$0.85 = \frac{746 \times 10^3}{\text{input}}$$

$$\text{input} =$$

$$\text{input} = 877.4 \text{ W} = 8.77 \text{ kW}$$

$$P = E_b \times I_a$$

$$I_a = \frac{P}{E_b}$$

$$= 5.776 \text{ kW}$$

Input power $P = V \times I_L$

$8.716 \times 10^3 = 400 \times I_L$
 $I_L = 19.46 A$

$I_f = \frac{V}{R_f} = 2.2 A$

$I_a = I_L - I_f$
 $= 17.26 A$

$E_b = V - I_a R_a$
 $E_b = 400 - 17.26 \times 0.8$

$E_b = 426.19 \text{ volts}$

Q3) 850 volt dc series motor has armature resistance of 0.08Ω and $R_f = 0.02 \Omega$ and produces full load torque when running at 500 rpm. If taking away of $40 A$ calculate I_a at speed when producing half of full load torque.

$V = 250$ $R_a = 0.08$ $R_f = 0.02$ $N_1 = 500 \text{ rpm}$
 $I_{a1} = 40 A$

$E_b I_a = T \propto \frac{N}{\omega}$

$V = I_a (R_a + R_f) + E_b$

$250 = 40 (0.08 + 0.02) + E_b$

$E_b = 246 V$

$246 \times 40 = \frac{T \times 12 \times 1500}{60}$

$T = 187.93$

$T \propto I_a^2$

$T_1 \propto 40^2 \rightarrow (1)$

$\frac{T_1}{2} \propto I_{a2}^2 \rightarrow (2)$

$I_{a2} = 28.28 A$

$E_b = \frac{P_g Z N}{60 A}$

$E_b \propto \phi N$ $\phi \propto I_a$

$E_b \propto I_a N$

$\frac{E_{b1}}{E_{b2}} = \frac{I_{a1} N_1}{I_{a2} N_2} \rightarrow (3)$

$E_{b1} = V - I_{a1} (R_a + R_s)$
 $= 250 - 40 (0.1)$
 $= 246 V$

$E_{b2} = 247.2 V$

by putting in eq (3)

$\frac{246}{247.2} = \frac{40 \times 500}{I_{a2} \times N_2}$

$N_2 = 710.66 \text{ rpm}$

I_a is only $5 A$

35 $Z = 540 \quad \phi = 30^\circ \text{ m.c.b}$
 $I_L = 1 \text{ A} \quad V = 220 \text{ V}$
 $P = 4 \text{ W} \quad R_a = 0.1 \Omega$

$I_L = 32 \text{ A}$
 $R_a = 5.6 \text{ k}\Omega$

$I_L = I_a + I_f$
 $82 = I_a + 1$
 $I_a = 81 \text{ A}$

$V = I_a R_a + E_b$
 $220 = 81 \times 0.1 + E_b$
 $E_b = 216.9 \text{ V}$

$T = 0.159 \sqrt{2 I_a P}$
 $= 0.159 \times \sqrt{2 \times 81 \times 216.9}$
 $= 0.159 \times 30 \times 540 \times 31 \times 10^{-3}$

$T = 79.849 \text{ Nm}$
 $E_b = 182 \text{ V}$
 $60 \times \text{A}$

$216.9 = \frac{4 \times 30 \times 10^{-3} \times 540 \times N}{60 \times 4}$
 $N = 803.33 \text{ rpm}$

$V = 220 \text{ V}$
 $I_L = 100 \text{ A}$

$N_1 = 700 \text{ rpm}$

$N_2 = 490 \text{ rpm}$

$T_1 = 0.7 T_2$

by 30% more

$T_2 = 0.7 T_1$

$R_a + R_{sa} = 0.1 \Omega$

$T \propto I_a^2$

$\frac{T_1}{T_2} = \left(\frac{I_{a1}}{I_{a2}} \right)^2$

$\frac{1}{0.7} = \left(\frac{100}{I_{a2}} \right)^2$

$I_{a2} = 83.66$

$E_{b1} = V - I_{a1} (R_a + R_{sc})$
 $= 220 - 100 (0.1)$

$E_{b1} = 210 \text{ V}$

$E_{b2} = V - I_{a2} (R_a + R_{sc})$

$E_{b2} = 211.63$

$\frac{E_{b1}}{E_{b2}} = \frac{I_{a1}}{I_{a2}} \frac{N_1}{N_2}$

$\frac{210}{211.63} = \frac{100}{N_2} \times \frac{700}{N_2}$

$N_2 = 705.43 \text{ rpm}$

$\frac{210}{211.63} = \frac{100}{83.66} \times \frac{700}{N_2}$

$N_2 = 843.21 \text{ rpm}$

$V = 24 \text{ V}$

$N = 1200 \text{ rpm}$

$I_L = 0.5 \text{ A}$

$R_a = 0.2 \Omega$

$I_L = I_a + I_f$
 $I_L = I_a$

$\frac{E_{b1}}{E_{b2}} = \frac{N_1}{N_2}$
 $\frac{23.9}{E_{b2}} = \frac{1200}{1120}$

$I_a = 0.5 \text{ A}$

$V = I_a R_a + E_b$

$E_{b1} = V - I_a R_a$

$= 24 - 0.5 \times 0.2$

$E_{b1} = 23.9 \text{ volts}$

$N_1 = 1200 \text{ rpm}$

$N_2 = 1120 \text{ rpm}$

$T \propto I_a$

$E_a \propto N$

$P = 24 \times 8.5$
 $P = 204 \text{ watt}$

$I_{a2} = 8.5 \text{ A}$

$E_{b2} = V - I_{a2} R_a$
 $22.3 = 24 - I_{a2} \times 0.2$