

4. TRANSISTOR CHARACTERISTICS

Date submitted : 03-04-2022 04:51:52

USN : 01FE21BEC268
Name : PRASHANTH SHIVAKUMAR ASKI
Department : Physics
Roll Number : 1736
Subject Name : Applied Physics Lab (ES)


Enter the Number of Observations : 9

INPUT CHARACTERISTICS:

SI Nos.	$V_{CE}=50V$		$V_{CE}=75V$		$V_{CE}=100V$	
	V_{BE} in(V)	I_B in (μA)	V_{BE} in(V)	I_B in (μA)	V_{BE} in(V)	I_B in (μA)
1	0	0	0	0	0	0
2	0.1	0	0.1	0	0.1	0
3	0.2	0	0.2	0	0.2	0
4	0.3	0	0.3	0	0.3	0
5	0.4	0	0.4	0	0.4	0
6	0.5	0	0.5	0	0.5	0
7	0.6	15	0.6	20	0.6	20
8	0.7	90	0.7	95	0.7	100
9	0.8	180	0.8	190	0.8	200

4. TRANSISTOR CHARACTERISTICS

Graph :

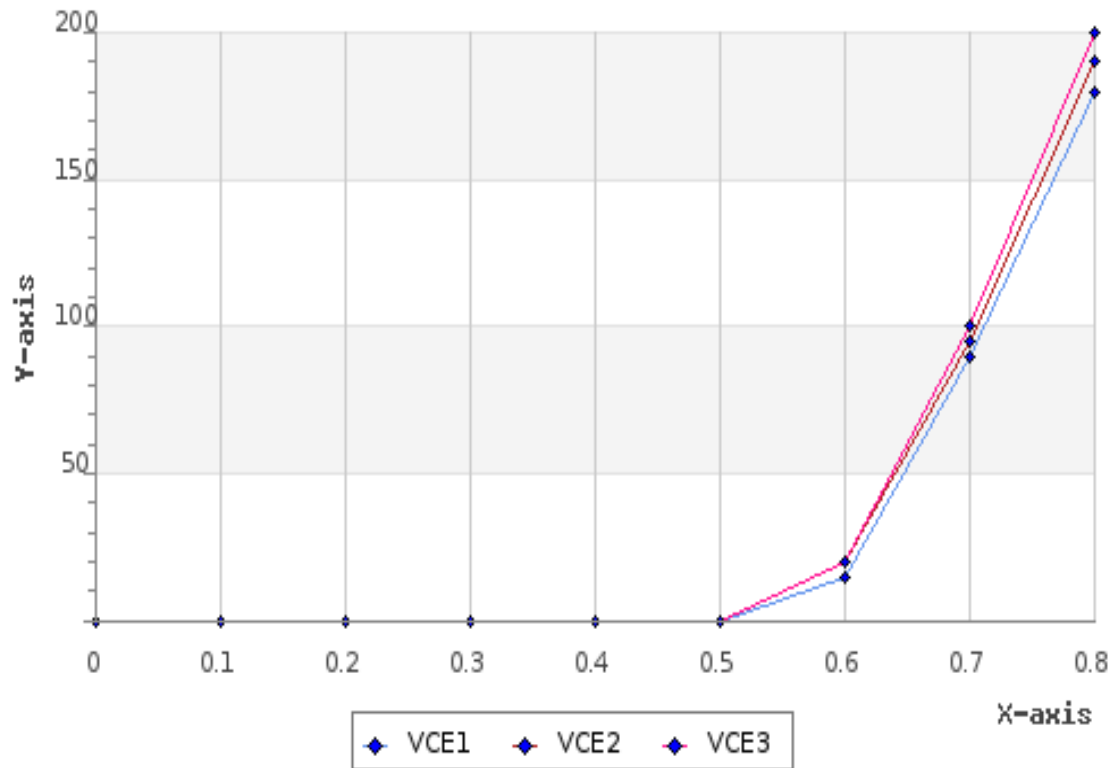

4. TRANSISTOR CHARACTERISTICS

Date submitted : 03-04-2022 04:51:52

USN : 01FE21BEC268
Name : PRASHANTH SHIVAKUMAR ASKI
Department : Physics
Roll Number : 1736
Subject Name : Applied Physics Lab (ES)


Enter the Number of Observations : 9

Variation of collected current I_B with V_{CE} at constant base Current I_B

SI	$I_B=50 \mu A$		$I_B=75 \mu A$		$I_B=100 \mu A$		$I_B=0 \mu A$		$I_B=0 \mu A$	
No.	V_{CE} in(V)	I_{CE} in(mA)	V_{CE} in(V)	I_{CE} in(mA)	V_{CE} in(V)	I_{CE} in(mA)	V_{CE} in(V)	I_{CE} in(mA)	V_{CE} in(V)	I_{CE} in(mA)
1	0	8.5	0	0	0	0	0	0	0	0
2	0.2	9	0.2	11.2	0.2	16	0	0	0	0
3	0.4	9	0.4	13	0.4	17	0	0	0	0
4	0.6	9	0.6	13	0.6	17	0	0	0	0
5	0.8	9	0.8	13	0.8	17	0	0	0	0
6	1	9	1	13	1	17	0	0	0	0
7	2	9	2	13	2	17	0	0	0	0
8	3	9	3	13	3	17	0	0	0	0
9	4	9	4	13	4	17	0	0	0	0


4. TRANSISTOR CHARACTERISTICS

Graph :

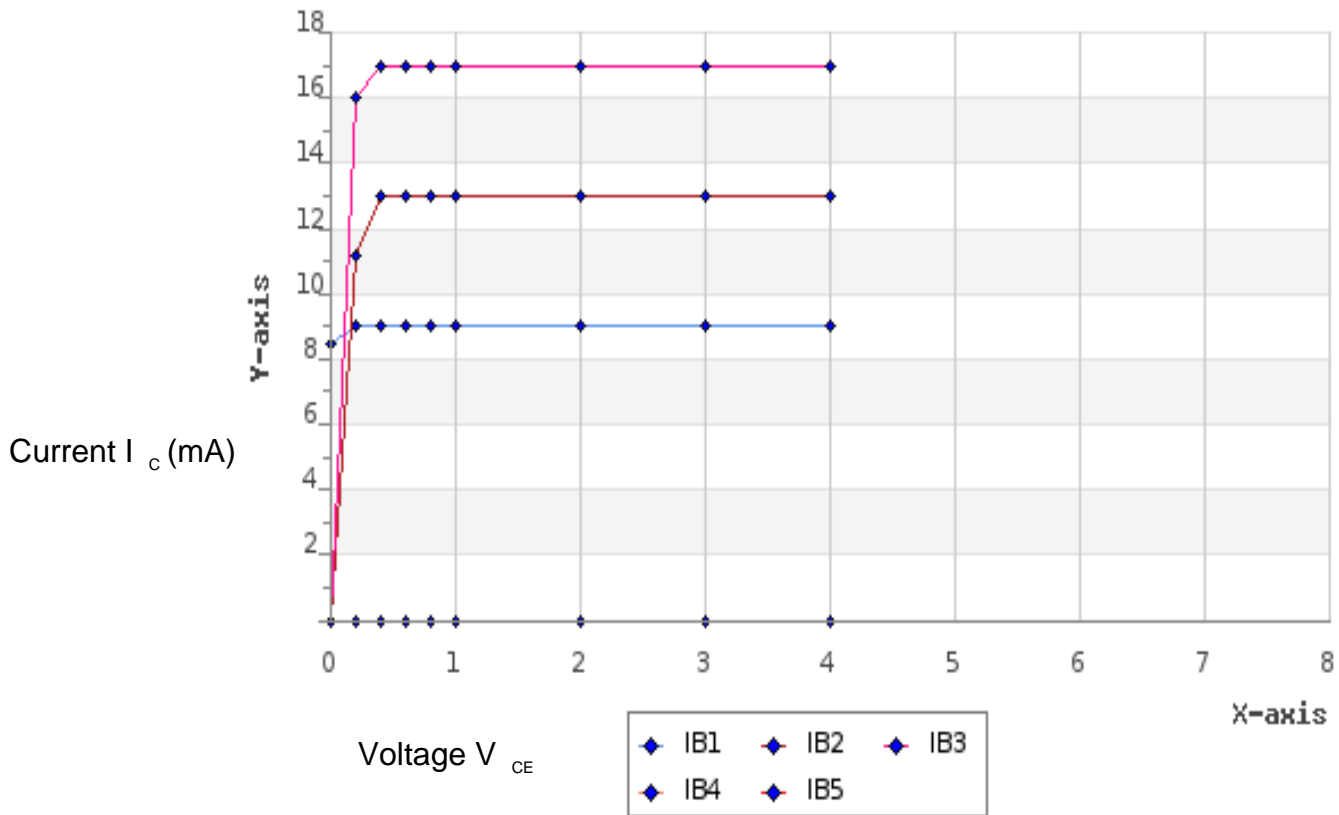

Saturated collector current with base current		
SI No	Base Current I_B in (μA)	Collector Current I_c (in mA)
1	50	9
2	75	13
3	100	17
4	0	0
5	0	0

4. TRANSISTOR CHARACTERISTICS

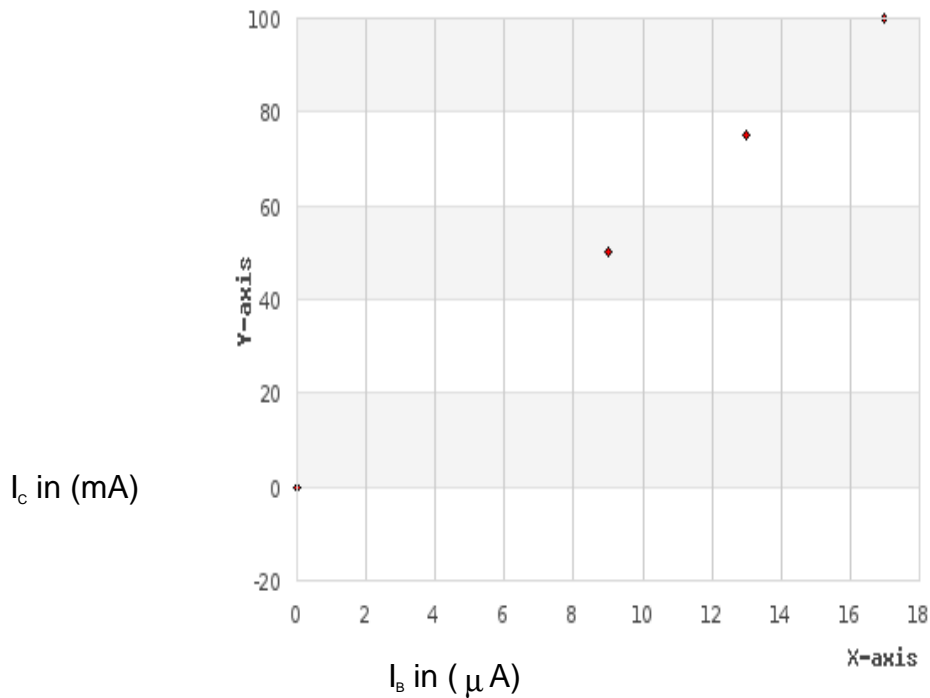

Results

The current amplification factor From graph $\beta = (\Delta I_C / \Delta I_B)_{V_{CE}} = 173$

Conclusion

The current amplification factor is the ratio of change in the collector current (ΔI_C) to the change in base current (ΔI_B) at a constant collector-emitter voltage (V_{CE}) and its value from the graph is 173.