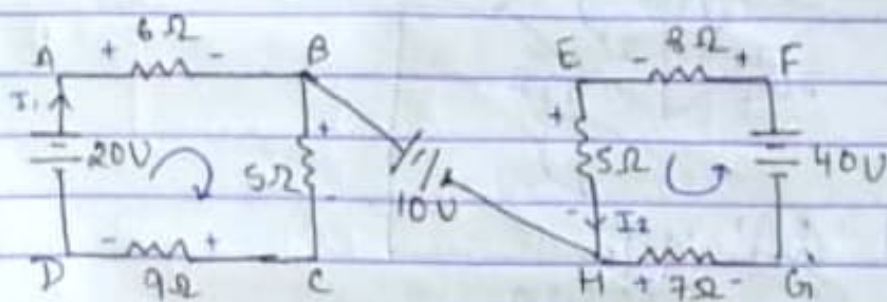


D.C. Circuits

REVIEW QUESTIONS:

- 1) For the given circuits below find the voltage across points C & F, & A & G



$$-6I_1 - 5I_1 - 9I_1 + 20 = 0$$

$$20 = 20I_1$$

$$\Rightarrow \boxed{I_1 = 1A}$$

$$-7I_2 + 40 - 8I_2 - 5I_2 = 0$$

$$40 = 20I_2$$

$$\boxed{I_2 = 2A}$$

$$\therefore \text{Now, } V_{CF} = V_F - V_C$$

$$V_{CF} = -8I_2 - 5I_2 + 10 - 5I_1$$

$$= -13I_2 + 10 - 5I_1$$

$$= -26 + 10 - 5$$

$$\boxed{V_{CF} = -21V}$$

$$\text{Now, } V_{AG} = V_G - V_A$$

$$+7I_2 + 10 + 6I_1 = V_{AG}$$

$$14 + 10 + 6 = V_{AG}$$

$$\boxed{V_{AG} = 30V}$$

$$+7 - I_1 - 2I_1 + I_2 + 2I_3 - 6 = 0$$

$$1 = 3I_1 - I_2 - 2I_3 \quad \text{--- (1)}$$

$$0 - I_2 - 2I_2 - 3I_2 + 3I_3 = 0$$

$$0 = 6I_2 - I_1 - 3I_3 \quad \text{--- (2)}$$

$$+6 - 3I_3 - I_3 - 2I_3 + 3I_2 + 2I_1 = 0$$

$$6 = 6I_3 - 3I_2 - 2I_1 \quad \text{--- (3)}$$

$$\begin{bmatrix} 1 \\ 0 \\ 6 \end{bmatrix} = \begin{bmatrix} 3 & -1 & -2 \\ -1 & 6 & -3 \\ -2 & -3 & 6 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

$$I_1 = 3A, I_2 = 2A, I_3 = 3A$$

Hence, current through

$$\text{Resistor 1} = I_1 - I_2 = 1A$$


$$\text{Resistor 2} = I_2 = 2A$$

$$\text{Resistor 3} = I_3 = 3A$$

$$\text{Resistor 4} = I_3 - I_2 = 1A$$

$$\text{Resistor 5} = I_1 - I_3 = 0A$$
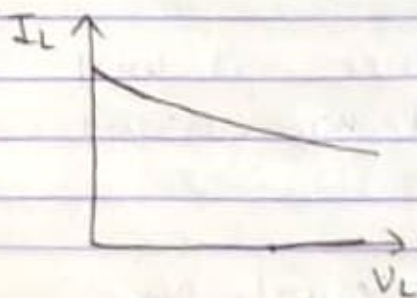
$$\therefore \text{current through shunt} = \frac{V_L}{R_{sh}}$$





$$I_s = \frac{V_L}{R_{sh}} + I_L$$

$$\therefore I_L = I_s - \frac{V_L}{R_{sh}}$$

where, I_L is the load current.

I_s is the source current.

Q6:- Determine the voltage V .

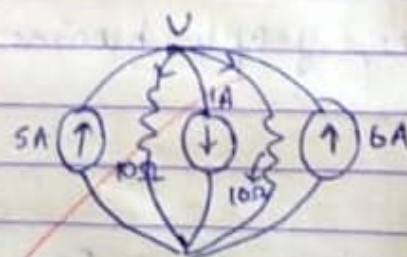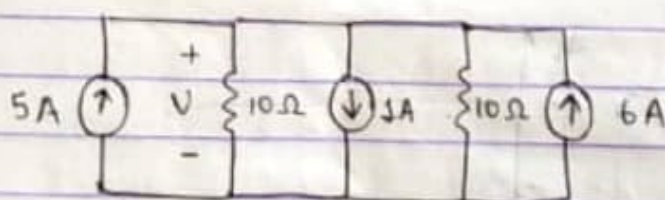


$$-5 - 6 + \frac{V}{10} + 1 + \frac{V}{10} = 0$$

$$\frac{2V}{10} = 10$$

$$V = 50V$$

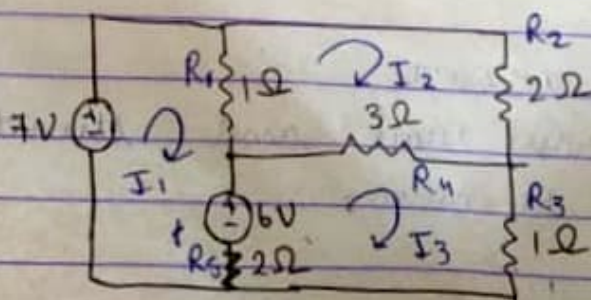Q7. Use mesh analysis to determine the current through each resistor.



1) Ideal case:- For ideal case of constant current generator, $R_{in} = 0$ $R_{sh} = \infty$.


Due to high value of resistance, it will behave as open circuit and no current will flow through it.

In ideal case, $R_{sh} = \infty$ so that equal am amount of current is supplied to all the loads.


$$\therefore \boxed{I_L = I_S}$$

where, I_L = load current


I_S = source current

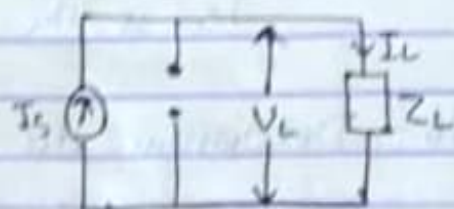

Hence, graph become

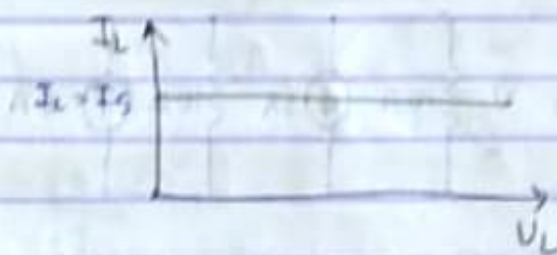

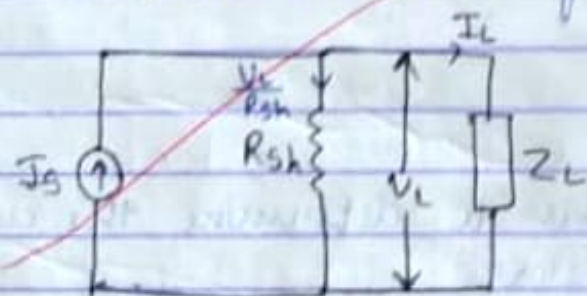2) Practical case:- For practical case of constant current generator, the shunt resistance ' R_{sh} ' will have some finite values.



Since it is a parallel circuits,

Hence, voltage across load and shunt resistance will be same.

Hence by applying KVL to the circuit, the source voltage V_s becomes

$$V_s = R_{in} I_L + Z_L \times I_L$$


Hence, I_L is the current through the source.

Since, load & R_{in} are


connected in series. Therefore,

the current through both of them will be same.


And Z_L is the impedance of load.

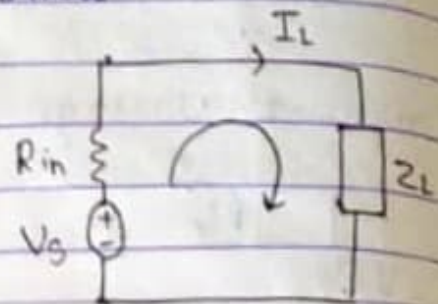

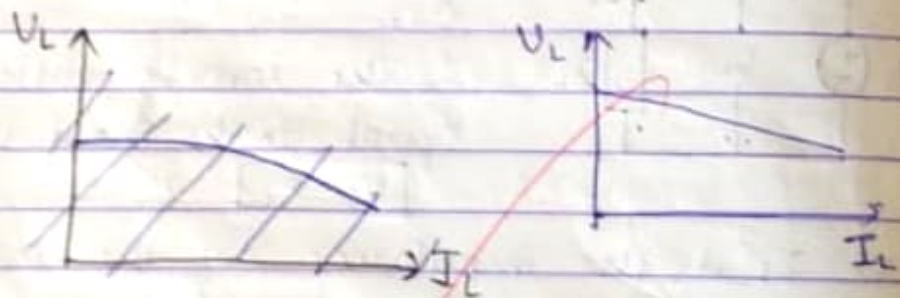Due to internal resistance of voltage source the graph of constant voltage generator in practical case becomes:




→ CONSTANT CURRENT GENERATOR:

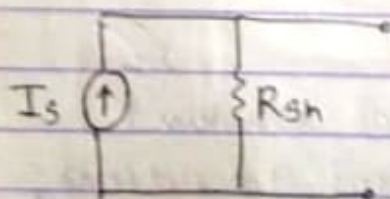

In constant current generator, a ~~shunt~~^{shunt} (resistance) is connected in parallel to the current source.

There are two cases of constant current generator:

4). Determine the node voltage.

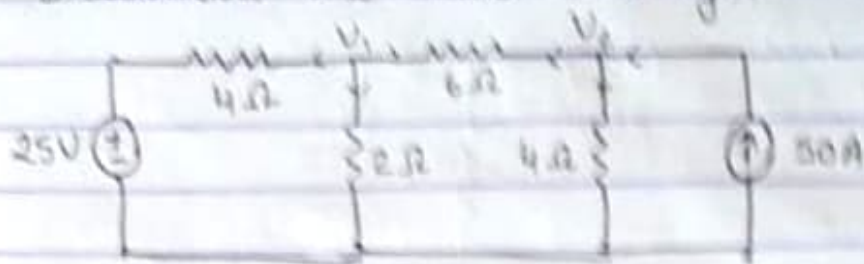

Applying KCL at node 1:-

$$\frac{V_1 - 25}{4} + \frac{V_1}{2} + \frac{V_1 - V_2}{6} = 0$$

$$V_1 \left(\frac{1}{4} + \frac{1}{2} + \frac{1}{6} \right) - \frac{V_2}{6} = \frac{25}{4} \quad \text{--- (i)}$$

Applying KCL at node 2:-

$$\frac{V_2 - V_1}{6} + \frac{V_2}{4} - 50 = 0$$

$$V_2 \left(\frac{1}{6} + \frac{1}{4} \right) - \frac{V_1}{6} = 50 \quad \text{--- (ii)}$$

Now, $I = 50V$

$$\begin{bmatrix} 25/4 \\ 50 \end{bmatrix} = \begin{bmatrix} 1/4 + 1/2 + 1/6 & -1/6 \\ -1/6 & 1/6 + 1/4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$


$$\begin{bmatrix} 6.25 \\ 50 \end{bmatrix} = \begin{bmatrix} 0.916 & -0.166 \\ -0.166 & 0.416 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$V_1 = 29.82V \approx 31V$$

$$V_2 = 131.66V$$

5) Explain constant voltage & constant current generators.

→ Constant voltage generator -

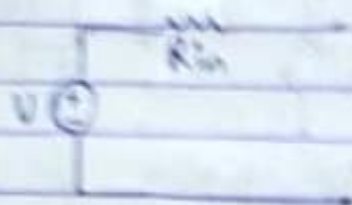

Two cases are there for constant voltage generators.

I. Ideal Case:



For ideal voltage source, the internal resistance becomes 0Ω .


\therefore The source voltage becomes equal to the load voltage

$$V_s = V_L$$

Here Z_L is the impedance of the load.

eg,


V_L	I_L	Z_L
10V	5A	2Ω
10V	2A	5Ω

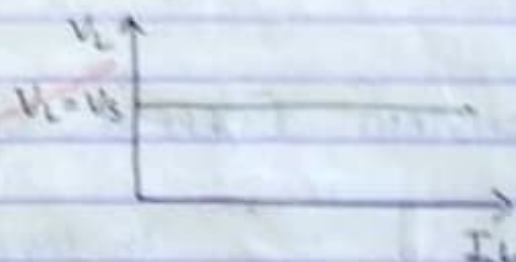

Hence, we can conclude that for a constant voltage generator, to be in ideal conditions, there will be constant voltage throughout the load.

II. Practical Case: In practical case, the voltage source have some internal resistance. Hence, by applying

3. Obtain node voltage V_1 & V_2

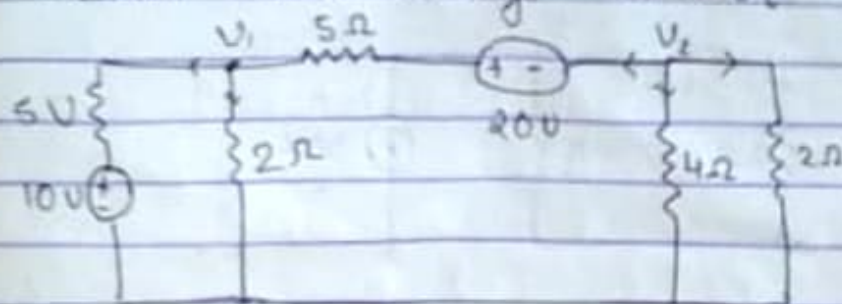

$$\frac{V_1 - 10}{5} + \frac{V_1}{2} + \frac{V_1 - 20 - V_2}{5} = 0$$

$$\frac{V_1}{5} + \frac{V_2}{2} + \frac{V_1}{5} - \frac{V_2}{5} = 6$$

$$V_1 \left(\frac{1}{5} + \frac{1}{2} + \frac{1}{5} \right) - \frac{V_2}{5} = 6 \quad \text{--- (1)}$$

Applying KCL at node -2 :- we get,

$$\frac{V_2}{2} + \frac{V_2}{4} + \frac{V_2 + 20 - V_1}{5} = 0$$

$$V_2 \left(\frac{1}{2} + \frac{1}{4} \right) + \frac{V_2}{5} - \frac{V_1}{5} = -4$$

$$V_2 \left(\frac{1}{2} + \frac{1}{4} + \frac{1}{5} \right) - \frac{V_1}{5} = -4 \quad \text{--- (2)}$$

Now, $I = 6V$

$$\begin{bmatrix} 6 \\ -4 \end{bmatrix} = \begin{bmatrix} 1/5 + 1/2 + 1/5 & -1/5 \\ -1/5 & 1/2 + 1/4 + 1/5 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} 6 \\ -4 \end{bmatrix} = \begin{bmatrix} 0.9 & -0.2 \\ -0.2 & 0.95 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$V_1 = 6.0122 \text{ V}$$

$$V_2 = -2.9447 \text{ V}$$

- 2) Find the current through the galvanometer 'G' in the wheatstone bridge shown in fig (a). Assume galvanometer resistance to be 5Ω .



For loop 1

$$20I_1 + 0 - 25I_1 - 5I_1 - 20I_1 + 5I_2 = 0$$

$$0 = 50I_1 - 5I_2 - 20I_3 \quad \text{--- (1)}$$

For loop 2:

$$0 - 10I_2 - 15I_2 - 5I_2 + 15I_3 + 5I_1 = 0$$

$$0 = -5I_1 + 30I_2 - 15I_3 \quad \text{--- (2)}$$

For loop 3

$$25 - 2I_3 - 20I_3 + 20I_1 - 15I_2 + 15I_2 - 2I_3 = 0$$

$$25 = 239I_3 - 20I_1 - 15I_2 \quad \text{--- (3)}$$

Using Mesh Analysis

$$\begin{bmatrix} 0 \\ 0 \\ 25 \end{bmatrix} = \begin{bmatrix} 50 & -5 & -20 \\ -5 & 30 & -15 \\ -20 & -15 & 39 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

$$I_1 = 0.539 \text{ A}$$

$$I_2 = 0.679 \text{ A}$$

$$I_3 = 1.179 \text{ A}$$

$$\therefore \text{Current through galvanometer} = I_2 - I_1$$

$$= 0.14 \text{ A}$$

A.C. CIRCUITS

Q1:- Define the terms: rms, average value, form factor of sinusoidal varying quantities
Sol:-

- rms value: It is defined as the root mean square value of an alternating quantity.

$$\begin{aligned} V_{rms} &= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V^2 d\theta} \\ &= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V_m^2 \sin^2 \theta d\theta} \\ &= \sqrt{\frac{V_m^2}{2\pi} \int_0^{2\pi} \left(\frac{1 - \cos 2\theta}{2} \right) d\theta} \\ &= \sqrt{\frac{V_m^2}{4\pi} \left[\theta - \frac{\sin 2\theta}{2} \right]_0^{2\pi}} \\ &= \sqrt{\frac{V_m^2}{4\pi} (2\pi - 0) - (\sin 2\pi - \sin 0)} \end{aligned}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$= 0.707 V_m$$

Similarly

$$I_{rms} = \frac{I_m}{\sqrt{2}} = 0.707 I_m$$

where $V_m = \text{max}^m \text{ voltage}$
 $I_m = \text{max}^m \text{ current}$

- Average Value: It is defined as the average of all instantaneous values during one alternation.

Average value for one completely cycle:

$$\begin{aligned} Avg &= \frac{1}{2\pi} \int_0^{2\pi} V \cdot d\theta \\ &= \frac{1}{2\pi} \int_0^{2\pi} V_m \sin \theta d\theta \end{aligned}$$

$$\begin{aligned}
 &= \frac{V_m}{2\pi} [-\cos\theta]_0^{2\pi} \\
 &= \frac{V_m}{2\pi} (\cos 0 - \cos 2\pi) \\
 &= \frac{V_m}{2\pi} (1 - 1) = 0
 \end{aligned}$$

Hence, average value i.e. V_{avg} for one complete cycle is 0.

For + Half Cycle:

$$\begin{aligned}
 Avg. &= \frac{1}{\pi} \int_0^{\pi} V \, d\theta \\
 &= \frac{V_m}{\pi} \int_0^{\pi} \sin\theta \, d\theta \\
 &= -\frac{V_m}{\pi} [\cos\theta]_0^{\pi} \\
 &= -\frac{V_m}{\pi} [\cos\pi - \cos 0] = -\frac{V_m}{\pi} [-1 - 1]
 \end{aligned}$$

$$\boxed{Avg. = \frac{2V_m}{\pi}} = 0.637 V_m$$

Similarly, $I_{avg} = 0.637 I_m$.

• form factor: It is defined as the ratio of the rms value to average value of an alternating quantity.

$$V_{rms} = 0.707 V_m$$

$$V_{avg} = 0.637 V_m$$

$$\therefore \text{form factor} = \frac{0.707 V_m}{0.637 V_m} = 1.11$$

Peak factor: It is defined as max^m value of to the rms value of an alternating quantity.

$$\text{Peak factor} = \frac{V_m}{0.707 V_m} = 1.414$$

- Q2. Obtain an expression for power in a series RL & RC circuits and also draw the phasor diagram and waveforms.



* RL-Circuit

Let us consider a circuit with 'V' as the rms voltage. There is a resistance 'R' and inductor with inductance 'L'. Since R & L are in series, the current through both will be same.

Now, let the voltage drop across 'R' be V_R & 'L' be V_L .

$$V_R = IR$$

$$V_L = IX_L$$

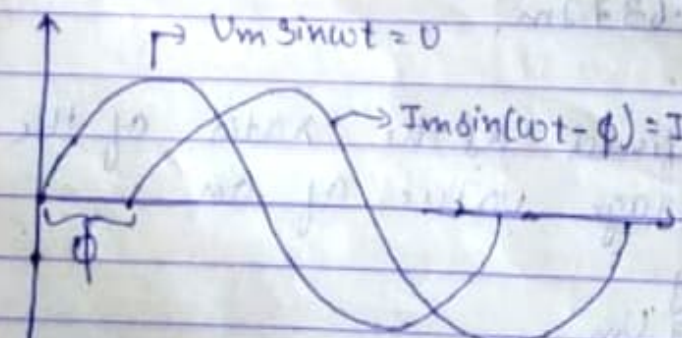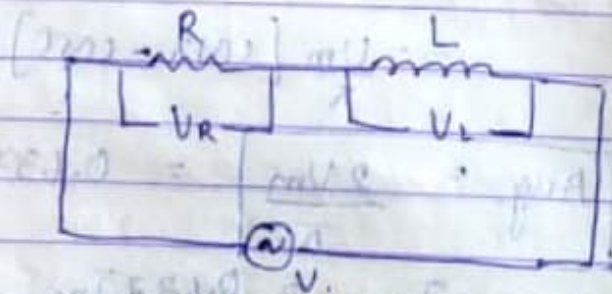


For a practical R-L circuit, current lags by ϕ .

Now, Power = $V \times I$

$$= V_m \sin \omega t \times I_m \sin(\omega t - \phi)$$

$$= V_m I_m \sin \omega t \sin(\omega t - \phi)$$
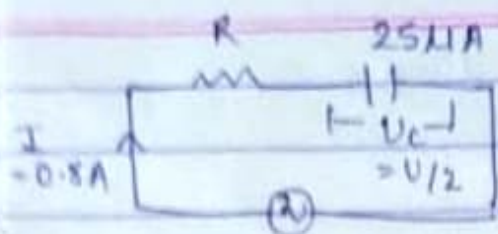
$$\sin A \sin B = \frac{1}{2} [\cos(A-B) - \cos(A+B)]$$



$$V_c = V/2$$

$$X_c = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 56 \times 25} = 127.323 \Omega$$

$$V_c = I X_c$$

$$\frac{V}{2} = \frac{0.8}{\pi} \times 10^6$$

$$V = 203.7183 V$$

$$\therefore V_c = \frac{203.71}{2} = 101.85 V$$

$$V = I Z$$

$$Z = \frac{V}{I} = \frac{203.17}{0.8}$$

$$= 254.625 \Omega$$

$$Z^2 = R^2 + X_c^2$$

$$64496.9514 = R^2 + 16211.38$$

$$R = 220.5 \Omega$$

$$\tan \phi = \frac{X_c}{R} = 0.5774$$

$$\phi = 30.0035^\circ$$

$$\cos \phi = 0.8659 \rightarrow \text{p.f. (leading)}$$

$$P = VI \cos \phi$$

$$= 203.71 \times 0.8 \times 0.8659$$

$$P = 140.15 \text{ Watts}$$

Let us consider two magnets which are acting as north pole & south pole. Three secondary coils i.e. RR' , YY' & BB' are suspended b/w the magnets.

In accordance with the Faraday's law of Electromagnetism, whenever a flux is cut inside the conductor an emf is said to be induced.

Hence, in fig 1, RR' cuts max^m flux & therefore max^m amount of voltage is induced in RR' .


Similarly in fig. ii, YY' will have max^m induced voltage & for fig. iii, BB' will have max^m induced voltage.

Hence, Instantaneous Voltage Equations can be written as:

$$V_R = V_m \sin \omega t$$


$$V_Y = V_m \sin(\omega t - 120^\circ)$$

$$V_B = V_m \sin(\omega t - 240^\circ)$$

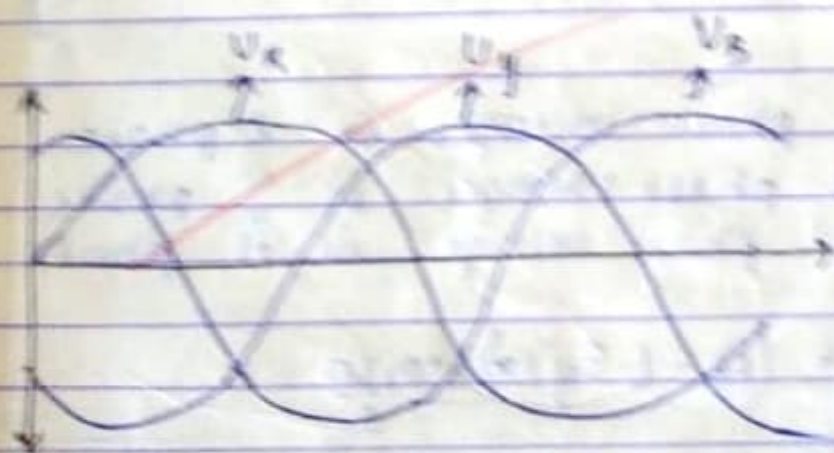

Q15. Derive the expression relationships b/w line & phase values of voltages & currents in star & delta connected balanced loads.

1. For STAR CONNECTION

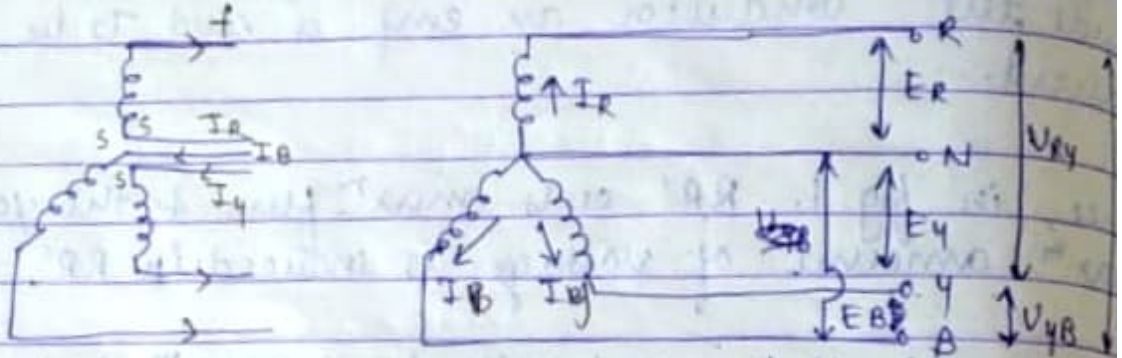


Now, line voltages can be written as -

$$V_{RY} = E_R - E_Y$$

$$V_{YB} = E_Y - E_B$$

$$V_{BR} = E_B - E_R$$

$$E_R = E_Y = E_B = E_{ph}$$

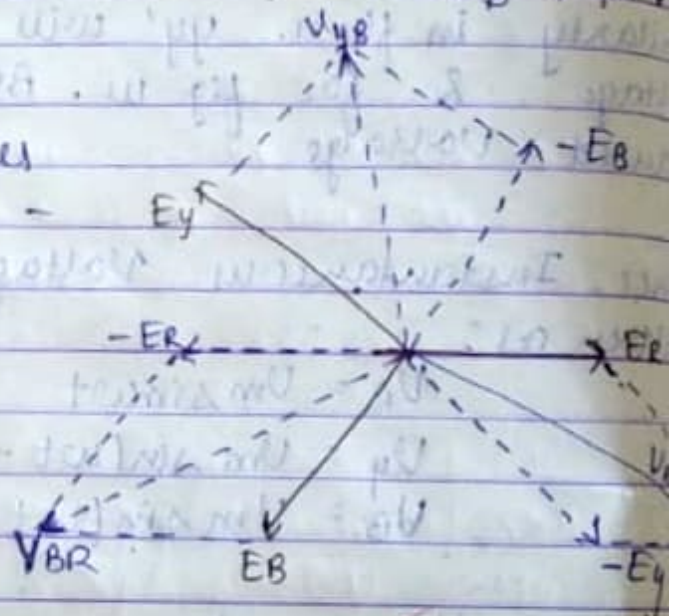

where,

E_R = induced phase voltages in R phase

E_Y = induced phase voltages in Y phase

E_B = induced phase voltage in B phase

Now,
$$V_{RY} = (E_R - (-E_Y)) \times \cos 60^\circ$$

$$= (E_R + E_Y) \cos 30^\circ$$

$$= 2 E_{ph} \times \frac{\sqrt{3}}{2}$$

$$\boxed{V_{RY} = \sqrt{3} E_{ph}}$$

For three phase

$$P = 3 \times I_{ph}^2 \times R$$

$$120 \times 10^3 = 3 \times (85)^2 \times R$$

$$R = \frac{120 \times 10^3}{3 \times (85)^2}$$

$$R = 5.53 \Omega$$

$$Z^2 = R^2 + X_L^2$$

$$Z_{ph} = \frac{V_{ph}}{I_{ph}} = \frac{635.08}{85} = 7.47 \Omega$$

$$V_L = \sqrt{3} V_{ph}$$

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{1100}{\sqrt{3}} = 635.08 V$$

$$\begin{aligned} X_L &= \sqrt{Z^2 - R^2} \\ &= \sqrt{(7.47)^2 - (5.5)^2} \\ &= 5.05 \Omega \end{aligned}$$

$$X_L = \frac{1}{2\pi f C} = 5.05 \Omega$$

$$C = \frac{1}{2\pi \times 50 \times 5.05} = 630 \mu F$$

$$\begin{aligned} \cos \phi &= R/Z \\ &= \frac{5.5363}{7.4715} \end{aligned}$$

$$\cos \phi = 0.7409 \text{ leading}$$

Q17. Three coils each of 16 Resistance & 12 inductive reactance are connected in delta across 400V, 50Hz supply. Determine

(vi) Power loss in each phase

$$P = I^2 R$$

$$= I_{ph}^2 \times R_{ph}$$

$$= (20)^2 \times 16$$

$$P_{loss} = 6400 \text{ Watts} \rightarrow \text{For 1 phase}$$

Total Power Loss

$$P_{Total} = 3 \times P_{loss}$$

$$= 3 \times 6400$$

$$= 19200 \text{ Watts}$$

Q18. Three inductive coils, each with a resistance of 10Ω & an inductance of 0.04 H are connected. i) in star ii) in delta to a 3-phase 400 V , 50 Hz supply. Calculate for each of the case a) phase current & line current & b) total power absorbed.

Delta Connⁿ.

$$R = 10 \Omega$$

$$L = 0.04 \text{ H}$$

$$X_L = 2\pi fL$$

$$= 2\pi \times 50 \times 0.04 \text{ V.P.} = 12.5663 \Omega$$

$$= 12.5663 \Omega$$

$$V_L = V_{ph}$$


$$I_L = \sqrt{3} I_{ph}$$

$$|Z_L| = \sqrt{(10)^2 + (12.5663)^2}$$

$$= 16.059 \Omega$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{400}{16.059} = 24.91 \text{ A}$$

$$Z_{ph}$$

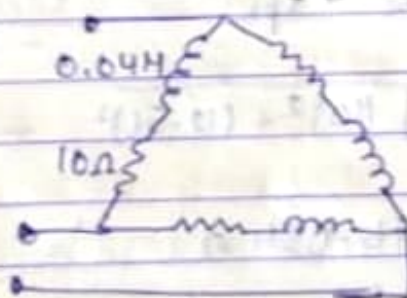

$$I_L = \sqrt{3} I_{ph}$$

$$= \sqrt{3} \times 24.91$$

$$= 43.155 \text{ A}$$

→ Power Absorbed

$$P = \sqrt{3} I_L V_L \cos \phi$$

$$= \sqrt{3} \times 43.155 \times 400 \times 0.62$$

$$= 18536 \text{ Watts}$$

$$\cos \phi = \frac{R}{Z}$$

$$\cos \phi = 0.62$$

→ In Star Connection

$$V_L = \sqrt{3} V_{ph}$$

$$I_L = I_{ph}$$

$$Z_{ph} = R_{ph} + jX_L$$

$$|Z_{ph}| = \sqrt{R^2 + X_L^2}$$

$$|Z_{ph}| = \sqrt{(10)^2 + (12.56)^2}$$

$$|Z_{ph}| = 16.059 \Omega$$



$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 230.9 \text{ V}$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{230.9}{16.059} = 14.38 \text{ A}$$

$$I_L = 14.38 \text{ A}$$

$$\cos \phi = R/Z = 10/16.059 = 0.62$$

Power consumed or absorbed

$$P = \sqrt{3} \times V_L I_L \cos \phi$$

$$= \sqrt{3} \times 400 \times 14.38 \times 0.62$$

$$= 6176.9 \text{ Watts}$$

$$\begin{aligned}\text{Now, } I_{L1} &= (I_R - (-I_B)) \cos 60^\circ/2 \\ &= (I_R + I_B) \cos 30^\circ \\ &= 2 I_{ph} \sqrt{3}/2 \\ \boxed{I_{L1} &= \sqrt{3} I_{ph}}\end{aligned}$$

$$\begin{aligned}I_{L2} &= (I_Y - (-I_R)) \cos 60^\circ/2 \\ &= 2 I_{ph} \times \sqrt{3}/2 \\ \boxed{I_{L2} &= \sqrt{3} I_{ph}}\end{aligned}$$

$$\begin{aligned}I_{L3} &= (I_B - (-I_Y)) \cos 60^\circ/2 \\ &= (I_B + I_Y) \cos 30^\circ \\ &= 2 I_{ph} \times \sqrt{3}/2 \\ \boxed{I_{L3} &= \sqrt{3} I_{ph}}\end{aligned}$$


In case of delta connectⁿ, line voltage is equal to phase voltage due to absence of neutral
 $\boxed{V_L = V_{ph}}$

Q16:- A balanced 3-ph star connected load of 120 kW takes a leading current of 85 A when connected across a 3-ph, 1100 V, 50 Hz supply. Obtain the values of resistance, impedance and capacitance of the load per phase & calculate the power factor of the load.

$$\begin{aligned}P &= 120 \text{ kW (load)} \rightarrow \text{load} \\ I_L &= 85 \text{ A} = I_{ph} \quad (\text{Star, } I_L = I_{ph}) \\ V &= 1100 \text{ V} \\ P &= 3 I_{ph}^2 R \rightarrow \text{Single Phase}\end{aligned}$$

- a) Impedance per phase b) phase current
 c) line current d) p.f. of the circuit
 e) phase difference f) power loss in each phase
 g) total power loss.

Qal:-

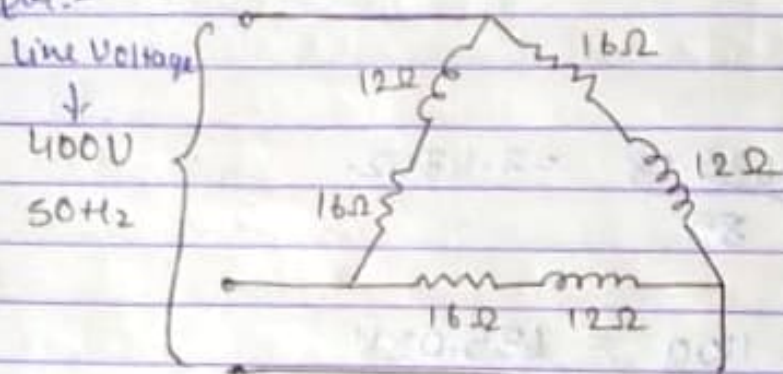

"In Delta Conn"

$$V_L = V_{ph} = 400V$$

$$Z_{ph} = R + X_L j$$

$$|Z_{ph}| = \sqrt{R^2 + X_L^2}$$

$$= \sqrt{(16)^2 + (12)^2}$$

$$= 20$$

$$Z_{ph} = 20 \Omega$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{400}{20} = 20A$$

$$I_L = \sqrt{3} I_{ph}$$

$$= 20\sqrt{3} A$$

$$I_L = 34.6A$$

$$\cos \phi = \frac{R}{Z}$$

$$\cos \phi = \left(\frac{16}{20} \right) = 0.8$$

$$\phi = \tan^{-1} \left(\frac{12}{16} \right) = 36.86^\circ$$

- $$V_{BR} = (E_B - (-E_R)) \cos 60/2$$

$$= (E_B + E_R) \cos 30^\circ$$

$$= 2 \times E_{ph} \times \sqrt{3}/2$$

$$V_{BR} = \sqrt{3} E_{ph}$$

- $$V_{YB} = (E_Y - (-E_B)) \cos 60/2$$

$$= (E_Y + E_B) \cos 30^\circ$$

$$V_{YB} = 2 \times E_{ph} \times \sqrt{3}/2$$


$$V_{YB} = \sqrt{3} E_{ph}$$

Now, for star connection line current are equal to the phase current.

Applying KCL, $I_R + I_Y + I_B = 0$
 $\therefore I_R = I_Y = I_B = I_{PL}$

where, I_R = current flowing through 'R' phase
 I_Y = current flowing through 'Y' phase
 I_B = current flowing through 'B' phase
 I_L = line current.

2. FOR DELTA CONNECTION -

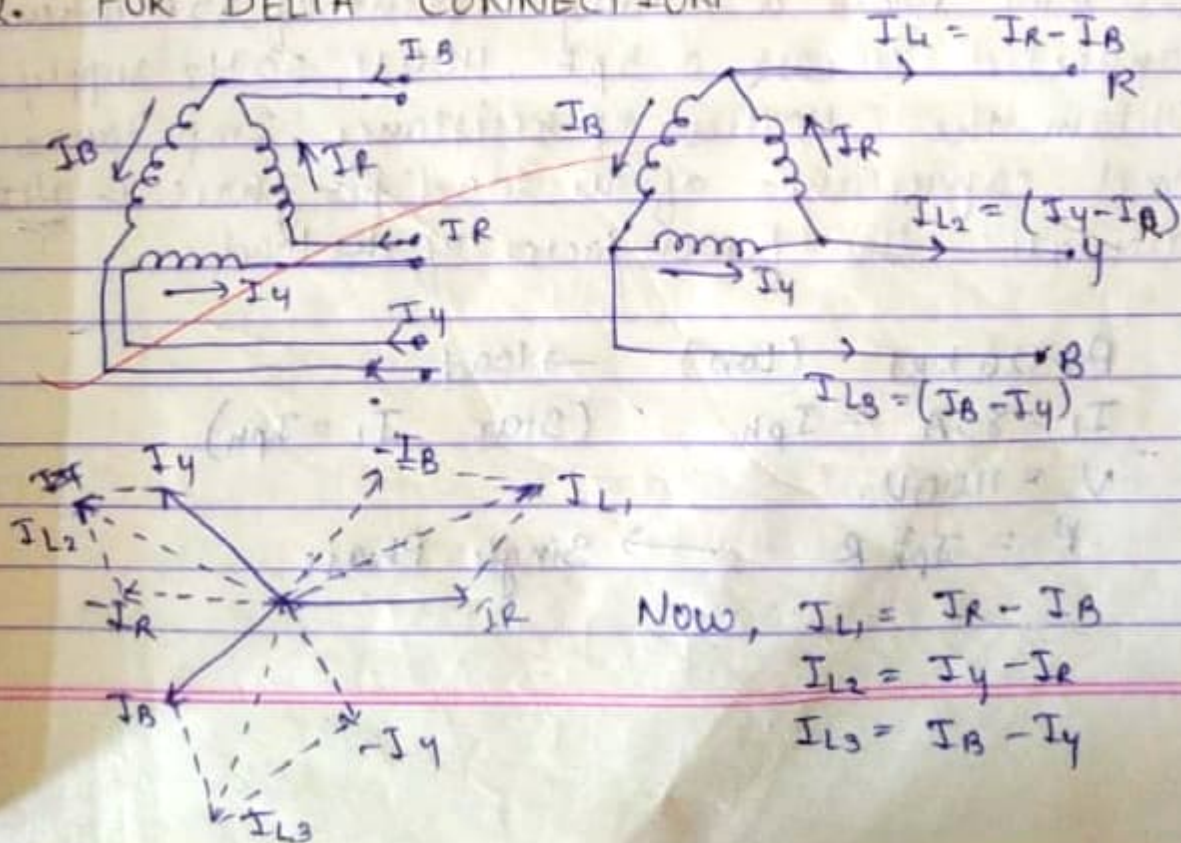

$$\cos \phi = 0.9839$$

$$P_{\text{total}} = 250 \times 33.1654 \times 0.983$$
$$= 8157.8592 \text{ Watts.}$$


Q13. List the advantages of 3 phases ac system over single phase ac systems;

1. Power factor of single phase AC motors, is lower than the three phase AC motor for same output & speed.
2. Single phase AC motors are not self-starting i.e. they require auxiliary apparatus for their starting but three phase AC motors are self starting.
3. For a given size, output of three phase AC machine is greater than the single phase supply motor.
4. For a given amount of power at a given voltage, 3 phase supply system requires $3/4^{\text{th}}$ weight of copper of single phase system.

Q14. Explain the generation of three phase voltages?

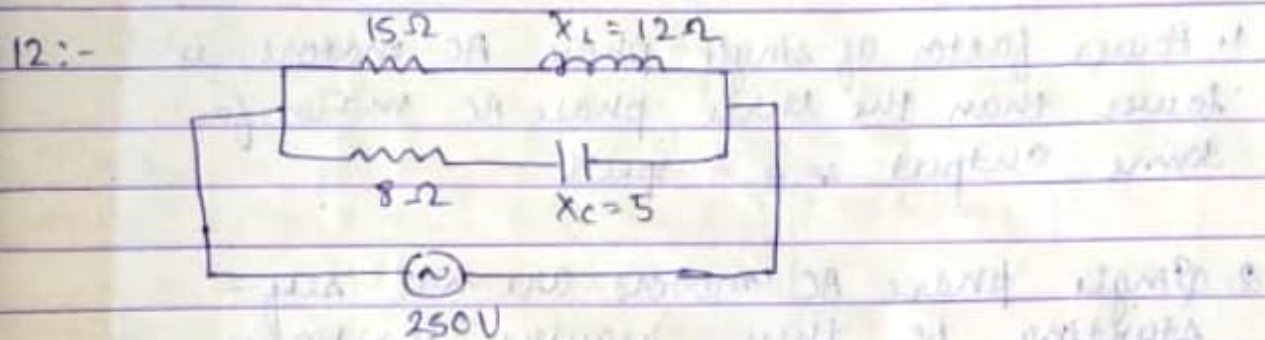Q12. Two impedances $Z_1 = 15 + j12 \Omega$ &
 $Z_2 = 8 - j5 \Omega$ are connected in parallel.
 if the potential difference across one of the
 impedance is 250V, calculate.

- total current & branch current.
- total power & power consumed in each branch
- Overall p.f.



$$Z_1 = 19.2093 \Omega$$

$$Z_2 = 9.433 \Omega$$

$$\therefore I_1 = \frac{V}{Z_1} = 13.0145 A$$

$$I_2 = 26.5001 A$$

$$\cos \phi_1 = \frac{15}{Z_1} = 0.7808$$

$$\cos \phi_2 = \frac{8}{Z_2} = 0.8480$$

$$I_R = I_1 \cos \phi_1 + I_2 \cos \phi_2$$

$$= 32.6339 A$$

$$I_R = I_2 \sin \phi_2 - I_1 \sin \phi_1$$

$$= 14.0449 - 8.1312$$

$$= 5.9137 A$$

$$I = \sqrt{I_R^2 + I_P^2} = 33.1654 A$$

$$P_1 = I_1 V \cos \phi_1 = 2540.4304 \text{ Watts}$$

$$P_2 = I_2 V \cos \phi_2 = 5618.0212 \text{ Watts}$$

$$P_{\text{total}} = P_1 + P_2$$

Now for resistance of the lamp -

$$P = \frac{V^2}{R} + \frac{100 \times 100}{R}$$

$$R = \frac{100 \times 100}{750} = \frac{40}{3} = 13.33 \Omega$$

Now Impedance of circuit:

$$Z = \frac{V}{I} = \frac{230}{7.5} = 30.67 \Omega$$

$$\text{Now } Z = \sqrt{R^2 + X_c^2}$$

$$X_c = \sqrt{Z^2 - R^2}$$

$$X_c = 27.62 \Omega$$

$$X_c = \frac{1}{2\pi fC} = \frac{1}{2 \times 3.14 \times 60} = 27.62$$

$$C = \frac{1}{2 \times 3.14 \times 60 \times 27.62}$$

$$= 960 \times 10^{-5}$$

$$= 96.0 \times 10^{-6} F$$

$$C = 96 \mu F$$

$$\text{Now, } \tan \theta = \frac{X_c}{R} \Rightarrow \theta = \tan^{-1} \left(\frac{27.62}{13.33} \right)$$

$$\theta = 64.21^\circ$$

Q11:- An adjustable resistor R in series with a capacitance of 25 μF draws a current of 0.8 A, when connected across 50 Hz supply. Calculate (i) the value of resistor so that the voltage across the capacitor is half the supply voltage (ii) the power, and (iii) p.f.

$$\begin{aligned}\text{Reactive Power} &= V \times I \times \sin \theta \\ &= 250 \times 22.36 \times \sin(63.4349) \\ &= 4999.84 \text{ VA}_r\end{aligned}$$

$$\begin{aligned}\text{Active Power} &= V \times I \times \cos \theta \\ &= 250 \times 22.36 \times 0.4472 \\ &= 2499.84 \text{ Watts}\end{aligned}$$

Q9. A two element series circuit consumes 400W & has p.f. = 0.707 leading. If applied voltage is $V = 141.4 \sin(314t + 30^\circ)$, find the circuit constants.

Sol:- P.f. = 0.707 leading

∴ The circuit consists a capacitor

∴ It is a R-C Network.

$$P = 700 \text{ W}$$

P.f. = 0.707 (Lead) → voltage is making 30°

$$V = 141.4 \sin(314t + 30^\circ) \text{ with reference.}$$

$$V = V_m \sin(\omega t)$$

$$\therefore V_m = 141.4$$

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}} = \frac{141.4}{\sqrt{2}} = 100 \text{ V}$$

$$V_{\text{rms}} = 100 \text{ V}$$

$$P = V_{\text{rms}} \times I_{\text{rms}} \times \cos \phi$$

$$400 = 100 \times I_{\text{rms}} \times 0.707$$

$$I_{\text{rms}} = \frac{4}{0.707} = 5.65 \text{ A}$$


$$\cos \theta = 0.707$$

$$\theta = \cos^{-1}(0.707)$$

$$\theta = 45^\circ$$

∴ Angle b/w voltage & current is 45° .

Here current leads because R-C network.

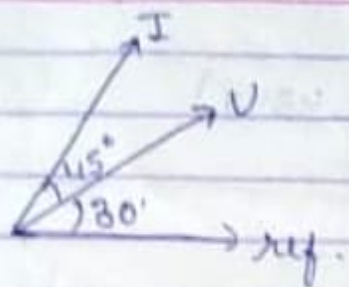

$$Z = \frac{V}{I} = \frac{(100 \angle 30^\circ)}{(9.9 \angle 75^\circ)}$$

$$= 7.1424 - 7.14j$$

$$Z = 10.10 \angle -45^\circ$$

$$314 = 2\pi f = \omega$$

$$f = \frac{314}{2\pi}$$

$$f = 50 \text{ Hz}$$


$$\therefore X_C = \frac{1}{2\pi f C}$$

$$C = \frac{1}{2\pi \times 50 \times 7.07}$$

$$C = 446 \mu\text{F}$$

Q10. A metal filament lamp rated at 750 W, 100 V & has p.f = 0.707 leading.

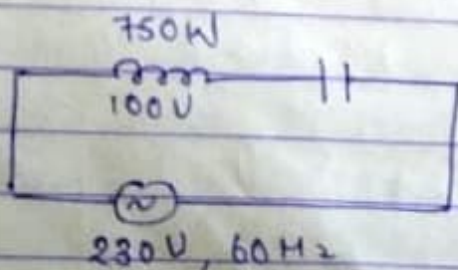Q10. A metal filament lamp rated at 750 W, 100 V is to be connected in series with a capacitor across a 230 V, 60 Hz supply. Calculate a) The capacitance required. b) The phase angle between current & supply voltage.



$$P = V \times I$$

$$I = \frac{P}{V} = \frac{750}{100} = 7.5 \text{ A}$$

$$I = 7.5 \text{ A}$$

$$(iv) P.F = \frac{R}{Z} = \frac{82}{71.43} = 0.447$$

$$\therefore \cos \theta = 0.447$$

$$(v) P = VI \cos \phi$$

$$= 240 \times 3.35 \times 0.447$$

$$= 359.388 \text{ Watts}$$

$$(vi) P_{\text{coil}} = V_{\text{coil}} \times I \times \cos \phi$$

$$\text{Here } \cos \phi = \frac{R}{Z} = \frac{12}{\sqrt{R^2 + X_L^2}} = \frac{12}{\sqrt{(144)^2 + (45.70)^2}} = 0.607$$

$$\therefore P_{\text{coil}} = 66.2 \times 3.35 \times 0.607 = 135.45 \text{ Watts}$$

Q8:- A voltage of 250V is applied to an inductive circuit of impedance $(5+j10)\Omega$. Calculate current, power factor, apparent & reactive power.

$$Z = 5 + j10$$

$$V = 250V$$

$$Z = \sqrt{25 + 100} = \sqrt{125} = 11.18 \Omega$$

$$Z = \frac{V}{I} \Rightarrow I = \frac{V}{Z} = \frac{250}{11.18} = 22.36$$

$$I = 22.36A$$


$$\tan \theta = \frac{X_L}{R} = \frac{10}{5} = 2$$

$$\theta = \tan^{-1}(2)$$

$$\theta = 63.4349^\circ$$

\therefore Power factor, $\cos \theta = 0.4472$
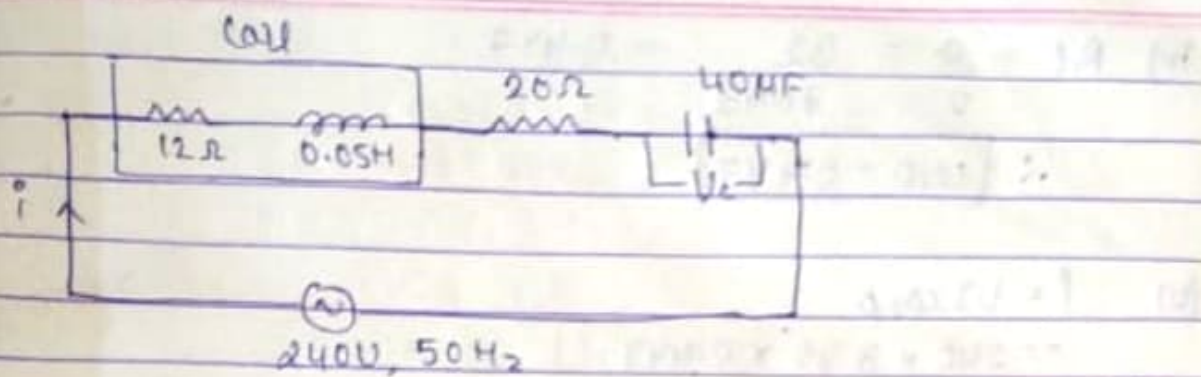
$$\begin{aligned} \text{Apparant Power, } &= V \times I \\ &= 250 \times 22.36 \\ &= 5590 \text{ VA} \end{aligned}$$



$$X_L = 2\pi f L = 2 \times \pi \times 50 \times 0.05$$

$$X_L = 15.70 \Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 40 \times 10^{-6}}$$

$$X_C = 79.57 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$= \sqrt{(32)^2 + (15.7079 - 79.5774)^2}$$

$$= 71.4374$$

$$I = \frac{240}{71.4374} = 3.35 \text{ A} \quad \text{--- (i)}$$

$$(ii) \quad V_{\text{coil}} = Z I \times Z_{\text{coil}}$$

$$= 3.35 \times \sqrt{R^2 + X_L^2} \quad I \in U = S$$

$$= 3.35 \times \sqrt{(12)^2 + (2\pi \times 0.05 \times 50)^2}$$

$$= 3.35 \times \sqrt{144 + 246.49} \quad I$$

$$= 3.35 \times 19.7608 \quad S = 01 = x = \text{mval}$$

$$= 66.19$$

$$\boxed{V_{\text{coil}} = 66.2 \text{ V}}$$

$$(iii) \quad V_C = I X_C$$

$$= 3.35 \times 79.57$$

$$= 266.5595 \text{ V} \quad I \times V = \text{mval} \text{ mval}$$

$$\boxed{V_C = 267 \text{ V}}$$

(b) $I = 96A$

$\therefore 96 = 120 \sin(2\pi ft)$

$\sin^{-1}(0.8) = 2\pi ft$

$53.130 = 2 \times \pi \times 60 \times t$

$t = \frac{53.13}{2 \times \pi \times 60}$

$t = 0.141$


$t = 0.141$

Q6:- when a certain inductive coil is connected to a dc supply at 240V, the current in the coil is 16A. when the same coil is connected to an ac circuit supply at 240V, 50Hz, the current is 12.27A. Calculate (i) resistance (ii) Impedance (iii) reactance & (iv) the inductance of the coil. If the supply were to be altered to 60Hz at 240V, then what happens to the current.

Frequency of DC supply is always 0.

$\therefore X_L$ has frequency component to it


$\therefore X_L = 2\pi fL = 0$

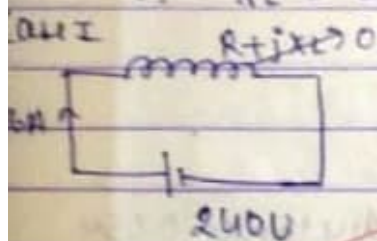

$\therefore R = \frac{V}{I} = \frac{240}{16} = 15 \Omega$

$R = 15 \Omega$ Resistance

Now, for AC supply.

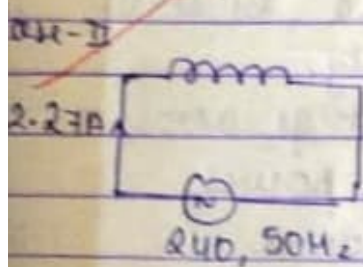

Now, $Z = \frac{V}{I} = \frac{240}{12.27} = 19.55 \Omega$

Impedance $Z = 19.55 \Omega$

Now,

$$Z = \sqrt{R^2 + X_L^2}$$

$$Z^2 = R^2 + X_L^2$$

$$X_L^2 = Z^2 - R^2$$

$$X_L = \sqrt{Z^2 - R^2}$$

$$= \sqrt{(19.55)^2 - (15)^2}$$

$$\boxed{X_L = 12.53 \Omega} \rightarrow \text{Reactance}$$

Now,


$$X_L = 2\pi fL$$

$$L = \frac{X_L}{2\pi f} = \frac{12.53}{2 \times 3.14 \times 50}$$

$$L = \frac{12.53}{314} = 0.0399$$

$$\boxed{L = 0.0399 \text{ H}} \rightarrow \text{Inductance}$$

Now,

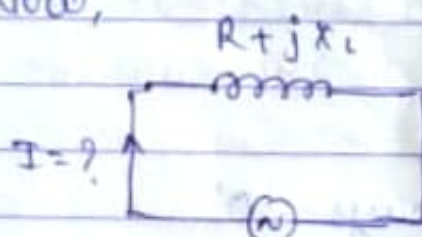

$$Z = \sqrt{R^2 + X_L^2}$$

$$= \sqrt{(15)^2 + (2 \times \pi \times 60 \times 0.0399)^2}$$

$$\boxed{Z = 21.26 \Omega}$$

240V, 60Hz

$$I = \frac{V}{Z} = \frac{240}{21.26} = 11.28 \text{ A}$$

Q7:- A coil of resistance 12Ω & inductance 0.05 H , a non-inductive resistor of 20Ω resistance & a loss-free $40 \mu\text{F}$ capacitor are connected in series across a $240\text{V}, 50\text{Hz}$ sinusoidal supply. Calculate a) the current, b) the voltage across the coil and the capacitor, c) the power consumed in the circuit, d) the power consumed by the coil and e) the power factor of the circuit.

- Active Power is the power dissipated in the circuit ~~resistance~~ given by $VI \cos \phi$. Its unit is Watts.

- Reactive Power is the power developed in the reactance of the circuit given by $VI \sin \phi$. Its unit is VAR.

- Apparent Power is the product of Voltage & current. Its unit is VA.

- Q5. An Alternating current of $f = 50 \text{ Hz}$ has a maximum value of 120 A . Write down the equation for its instantaneous value. Reckoning time from the instant the current is zero and is becoming positive, find
- (a) instantaneous value after $1/360 \text{ sec}$.
 - (b) the time taken to reach 96 A for the first time.

$$f = 60 \text{ Hz}$$

$$I_m = 120 \text{ A}$$

$$I = I_m \sin \omega t$$


$$I = 120 \sin (\pi f t)$$

(a) $t = \frac{1}{360} \text{ sec}$

$$I = 120 \sin \left(2\pi \times 60 \times \frac{1}{360} \right)$$

$$= 120 \sin (\pi/3)$$

$$\boxed{I = 103.92 \text{ A}}$$

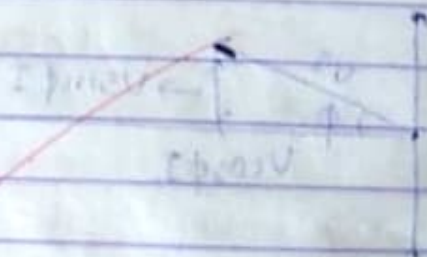


Importance Of Power factor -

- If the value of power factor is in b/w 0.8 to 1 then it is ideal case.
- The value of power factor should be kept as high as possible in the circuit so that the angle b/w current & voltage is less and they become as near as possible.
- Low Power factor causes high voltage loss & power loss in the line, & thus decreasing the line efficiency.
- Power factor of 1 is preferred by electric board also. If it is less than that then they have to supply more current for a given power use & thus more power loss.

Q4. Define active and reactive power in a A.C. circuit.

Let 'I' be the reference quantity.

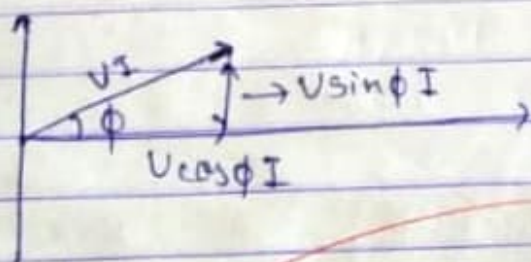

Resolve 'V' into two components along x-axis as well as y-axis. Since, 'I' is the reference quantity. Hence we multiply every side by I.

$$\begin{aligned} \therefore VI \cos \phi &\rightarrow \text{Active Power} \\ VI \sin \phi &\rightarrow \text{Reactive Power} \\ VI &\rightarrow \text{Apparent Power} \end{aligned}$$

$$AP/PF = I$$

$$P = \frac{V_m I_m}{2} [\cos(\omega t - \omega t + \phi) - \cos(\omega t - \omega t + \phi)]$$

$$= \frac{V_m I_m}{2} [\cos \phi - \cos(2\omega t - \phi)]$$

It varies from 0 to 2π & avg. value of one complete cycle is 0.

\therefore It will not contribute anything to the power

$$P = \frac{V_m I_m \cos \phi}{2}$$

$$\therefore V_{rms} = \frac{V_m}{\sqrt{2}} ; I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$\therefore \boxed{P = V_{rms} I_{rms} \cos \phi}$$


Phasor Diagram:

$$V = V_R + V_L$$

$$V = IR + IX_L$$


$$V = I(R + X_L)$$
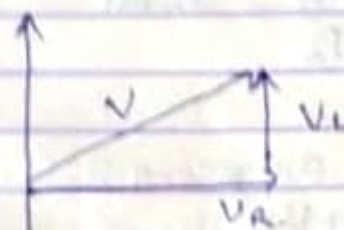
$$V/I = R + X_L \Rightarrow \boxed{Z = R + X_L}$$




* RC- Circuit

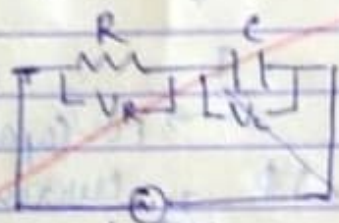Let us consider a circuit with rms voltage as 'V'. There is a resistance 'R' & capacitor 'C'. Since, both are connected in series hence current through both will be same. Let voltage drop across the resistance be 'V_R' & capacitor be 'V_C'.



$$V_R = IR$$

$$V_C = IX_C$$

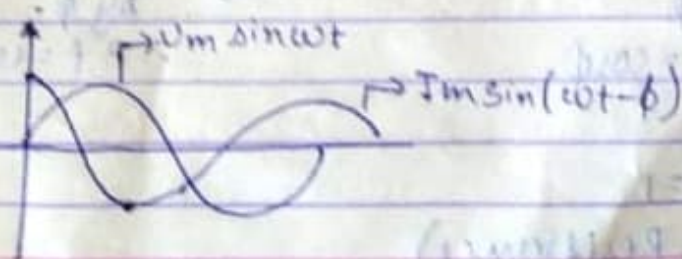

$$\begin{aligned}
 P &= VI \\
 &= V_m \sin \omega t \cdot I_m (\sin (\omega t + \phi)) \\
 &= V_m I_m \sin \omega t \sin (\omega t + \phi) \\
 &= \frac{V_m I_m}{2} [\cos \phi]
 \end{aligned}$$

$$P = V_{rms} I_{rms} \cos \phi$$

$$\therefore V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$\frac{I_m}{\sqrt{2}} = I_{rms}$$


• Phasor diagram:

$$V = V_R + V_c$$

$$V = IR - IX_c$$



$$V/I = R - jX_c$$

$$Z = (R - jX_c)$$

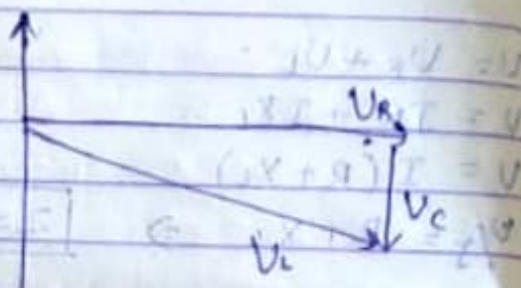

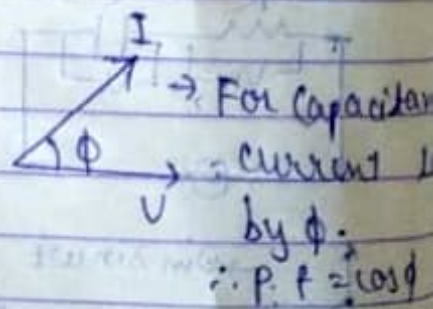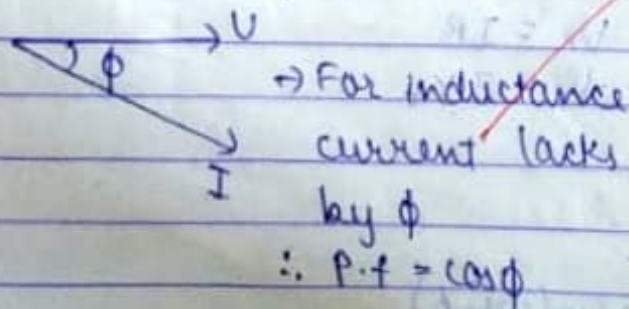Q3. Define power factor and explain the importance of power factor.

- Power factor of an alternating circuit is defined as the cosine of angle b/w the current and the voltage.
- It is also defined as the ratio of resistor to the impedance.



$$\cos \phi = 1 \quad (\text{For Resistance})$$