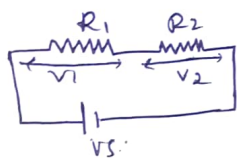


CHAPTER 2 :- D. C. Circuits.

1) Voltage Divider Rule:



$$V = IR$$

$$V_S = V_1 + V_2$$

$$I R_S = I R_1 + I R_2$$

$$\boxed{R_S = R_1 + R_2}$$


$$V_1 = I R_1$$

$$= \frac{V_S \times R_1}{R_1 + R_2}$$

$$V_2 = \frac{I R_2}{R_1 + R_2}$$

$$V_2 = \frac{V_S R_2}{(R_1 + R_2)}$$

2) Current divider Rule

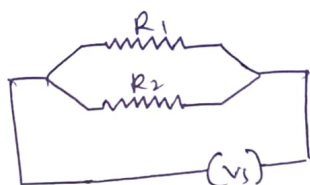

$$V_P = V_1 = V_2$$

$$I = I_1 + I_2$$

$$\frac{V}{R_P} = \frac{V_1}{R_1} + \frac{V_2}{R_2}$$

$$\frac{V}{R_P} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$I_1 = \frac{V}{R_1}$$

$$= \frac{I (R_1 R_2)}{R_1 (R_1 + R_2)} = \frac{I R_2}{(R_1 + R_2)}$$

$$I_2 = \frac{V}{R_2} = \frac{I (R_1 R_2)}{(R_1 + R_2) R_2} = \frac{I R_1}{(R_1 + R_2)}$$

Kirchoffs laws

1) Kirchoff's Junction law

at particular junction, sum of incoming currents is equal to out going current.


$$I_1 = I_2 + I_3 \rightarrow I_1 - I_2 - I_3 = 0$$

2) Kirchoff's voltage law.


at any instant in a closed loop the algebraic sum of EMF's acting around the loop is equal to the algebraic sum of potential drop/difference round the loop.

→ Sign Conventions


a) Sign of battery EMF

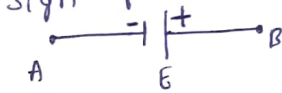

b) Sign of voltage drop across resistor

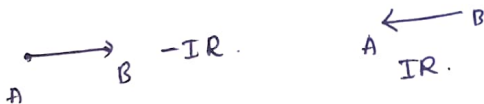

Example:

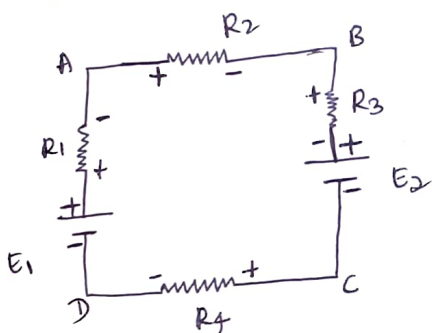

$$-IR_2 - IR_3 - E_2 - IR_4 + E_1 - IR_1 = 0$$

$$-I(R_1 + R_2 + R_3 + R_4) = E_2 - E_1$$

X by (-)


$$I(R_1 + R_2 + R_3 + R_4) = E_1 - E_2$$

Numericals:

A simple circuit is formed using 12V lead acid battery and automobile headlight. The battery delivers a total energy of 460.8 J watt hour over an 8 hr. discharge period.

a) How much power is delivered to the headlight.

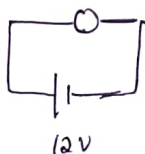b) What is the current flowing through the bulb
(assume battery voltage remains constant during discharge)



$$a) \text{ power} = \frac{E}{t} = \frac{460.8 \text{ watt hr}}{8 \text{ hr}}$$

$$P = 57.6 \text{ W}$$


$$b) P = V \times I$$

$$57.6 = 12 \times I$$

$$I = \frac{57.6}{12}$$

$$I = 4.8 \text{ A}$$

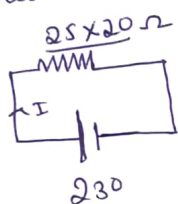- 2) The lamps in a set of Christmas are connected in series. If there are 20 lamps and each lamp has resistance of 25Ω . Calculate the (a) total resistance of set of lamps and hence calculate the current and power taken from 230V supply




a) $T_R = 500 \Omega$

b) current $I = \frac{230V}{500} = 0.46$ A

c) power $= V \times I = 230 \times 0.46$
 $= 23 \times 4.6$
 $= 105.8 \text{ W}$

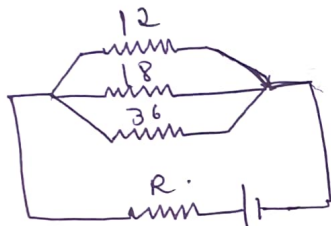- 3) A circuit comprising of 3 resistances, 12Ω , 18Ω , 36Ω joined in parallel is connected in series with 4th resistance. The whole circuit is supplied at 60V and it is found that the power dissipated in the 12Ω resistance is 36W. Determine value of 4th resistance and total power dissipated in the group



$$\frac{1}{R_{eq}} = \frac{1}{12} + \frac{1}{18} + \frac{1}{36}$$

$$\frac{1}{R_{eq}} = \frac{3 + 2 + 1}{36} = \frac{6}{36} = \frac{1}{6}$$

$$R_{eq} = 6 \Omega$$

$$I = \frac{V}{R+6}$$

$$V = I(R+6)$$

$$60 = I(R+6)$$

p in 12Ω

$$p = V_1 \times I_1$$

$$36 = 6I \times I_1$$

$$I_1 = \frac{6}{I}$$

$$60 = IR + I(6)$$

$$60 = I(6+R)$$

$$I = \frac{60}{(6+R)}$$

$$P_{12} = \frac{V^2}{R}$$

$$36 = \frac{V^2}{12}$$

$$36 \times 12 = V^2$$

$$V = \sqrt{36 \times 12}$$

$$= 6\sqrt{12}$$

$$V = 12\sqrt{3} \text{ V}$$

$$I_1 R^2 = I_2^2 = \frac{6}{36} I_3$$

$$2I_1 = 3I_2 = 6I_3$$

$$I_2 = I_1 \frac{2}{3}, I_3 = \frac{I_1}{3}$$

$$I_1 = \frac{12\sqrt{3}}{12} = 1.73$$

$$I_2 = \frac{12\sqrt{3}}{18} = 1.15$$

$$I_3 = \frac{12\sqrt{3}}{36} = \frac{1}{\sqrt{3}} = 0.57$$

$$I = 3.45$$


$$P_T = V \times I$$

$$= 60 \times 3.45$$

$$= 207 \text{ W}$$

power dissipated in parallel group = $12\sqrt{3} \times 3.45$
 $= 71.706 \text{ W}$


4)

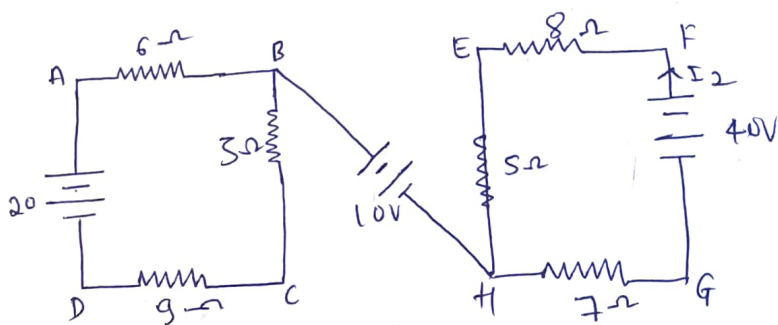

Crucial

For the given, voltage across points C & F and A & G

1) C and F

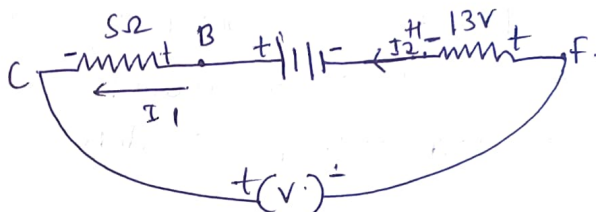

$$V_{CF} + I_1 \times 5 + 13I_2 - 10 = 0$$

$$V_{CF} + I_1 \times 5 + 13I_2 = 10$$


$$V_{CF} + 5 \times 1 + 13 \times 2 = 10$$

$$V_{CF} = 10 - 26 - 5$$

$$V_{CF} = 10 - 31$$

$$V_{CF} = -21 \text{ V}$$

2) A and G

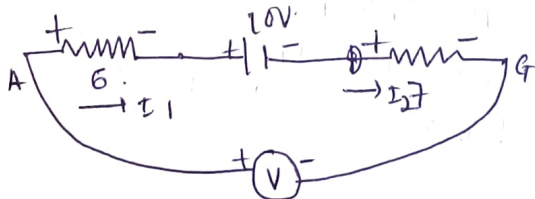

$$V_{AG} - 6I_1 - 10 - I_2 \times 7 = 0$$

$$V_{AG} = 6I_1 + 10 + 7I_2$$

$$= 6 \times 1 + 10 + 7 \times 2$$


$$= 6 + 10 + 14$$

$$= 16 + 14$$

$$V_{AG} = 30 \text{ V}$$

Maxwell's Circulating Current Method / Maxwell's Loop Current Method

1) Step 1: Identify number of meshes

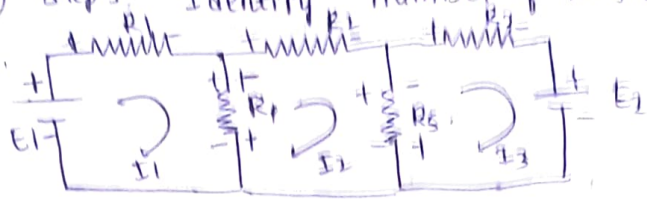

2) Step 2: Assign the current in clockwise direction for each mesh.

Step 3: Apply KVL for each mesh

Mesh 1:

$$-I_1 R_1 - I_1 R_4 + I_2 R_4 + E_1 = 0$$

$$E_1 = I_1 (R_1 + R_4) - I_2 R_4$$

Mesh 2:

$$-I_2 R_2 - I_2 R_5 + I_3 R_5 - I_2 R_4 + I_1 R_4 = 0$$

$$0 = I_1 R_4 + I_3 R_5 - I_2 (R_2 + R_5 + R_4)$$

Mesh 3:

$$-I_3 R_3 - E_2 - I_3 R_5 + I_2 R_5 = 0$$

$$-E_2 = I_3 R_5 + I_3 R_3 - I_2 R_5$$

$$-E_2 = I_3 (R_5 + R_3) - I_2 R_5$$


Step 4:

Matrix form

$$V = RI$$

$$\begin{bmatrix} E_1 \\ 0 \\ E_2 \end{bmatrix} = \begin{matrix} & \begin{matrix} 1 & 2 & 3 \end{matrix} \\ \begin{matrix} 1 \\ 2 \\ 3 \end{matrix} & \begin{bmatrix} R_1 + R_4 & -R_4 & 0 \\ -R_4 & R_2 + R_4 + R_5 & -R_5 \\ 0 & -R_5 & R_3 + R_5 \end{bmatrix} \end{matrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

1)

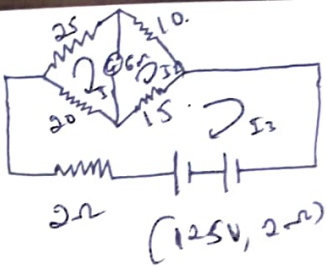

find the current through the galvanometer 'G' in the Wheatstone bridge in figure. Assume $G = 5\Omega$

$$V = RI \quad \begin{matrix} 1 & 2 & 3 \end{matrix}$$

$$\begin{bmatrix} 0 \\ 0 \\ 25 \end{bmatrix} = \begin{bmatrix} 25+5+20 & -5 & -20 \\ -5 & 10+20 & -15 \\ -20 & -15 & 20+15+4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

$$\begin{bmatrix} 0 \\ 0 \\ 25 \end{bmatrix} = \begin{bmatrix} 50 & -5 & -20 \\ -5 & 30 & -15 \\ -20 & -15 & 39 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$


$$I_1 = 0.54 \quad I_2 = 0.68, \quad I_3 = 1.18$$

$$I_2 > I_1$$

$$I_G = 0.68 - 0.54 = 0.14 \text{ A}$$

$$I_G = 0.14 \text{ A}$$

2)

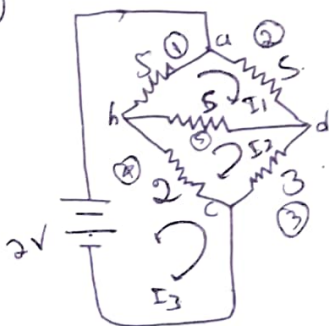

use mesh analysis to determine the current through each resistor and determine the voltage across A and C and b & d.

$$V = RI$$

$$\begin{bmatrix} 0 \\ 0 \\ 2 \end{bmatrix} = \begin{bmatrix} 15 & -5 & -5 \\ -5 & 10 & -2 \\ -5 & -2 & 7 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

$$I_1 = 0.26 \text{ A}$$

$$I_2 = 0.24 \text{ A}$$

$$I_3 = 0.54 \text{ A}$$

Current through 1st resistor

$$I_1 - I_3 = 0.26 - 0.54 = -0.28$$

Current through 5th resistor

$$I_1 - I_2 = 0.02 \text{ A}$$

Current through 2nd resistor & 3rd resistor


$$I_1 = 0.26 \text{ A}$$

$$I_3 = 0.24 \text{ A}$$

Current through 4th resistor

$$I_3 - I_2 = 0.54 - 0.24 = 0.30 \text{ A}$$

V. across A & C & b & d.

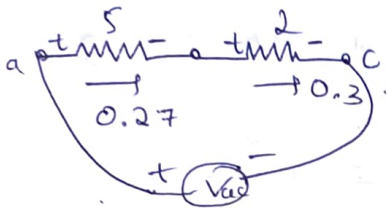

$$V_{AC} - 5 \times 0.27 - 0.3 \times 2 = 0$$

$$V_{AC} = 5 \times 0.27 + 0.3 \times 2$$

$$= 1.35 + 0.6$$


$$V_{AC} = 1.95 \text{ V}$$

$$V_{BD} = (I_1 - I_2) \times 5$$

$$= 0.02 \times 5$$

$$= 0.10 \text{ V}$$

3)

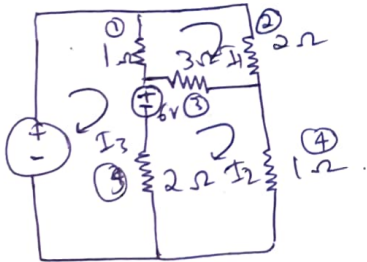

we mesh analysis to find current in each resistor

$$V = RI$$

$$\begin{bmatrix} 0 \\ 6 \text{ V} \\ 1 \end{bmatrix} = \begin{bmatrix} 3+2+1 & -3 & -1 \\ -3 & 3+2+1 & -2 \\ -1 & -2 & 1+2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

$$\begin{bmatrix} 0 \\ 6 \\ 1 \end{bmatrix} = \begin{bmatrix} 6 & -3 & -1 \\ -3 & 6 & -2 \\ -1 & -2 & 3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

$$I_1 = 2 \quad I_2 = 3 \quad I_3 = 3$$

$$\text{5th } R = 3 \text{ A} - 2 = 1 \text{ A}$$

$$\text{2nd } R = 2 \text{ A}$$

$$\text{3rd } R = I_1 - I_2 = 2 - 3 = -1 \text{ A}$$


$$\text{4th } R = 3 \text{ A}$$

$$\text{5th } R = I_3 - I_2$$

$$= 3 - 2$$

$$= 1 \text{ A}$$


Nodal Analysis:

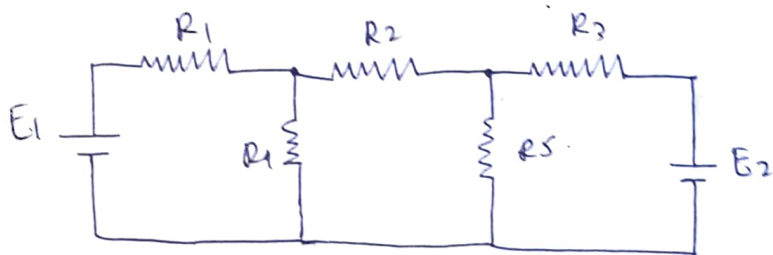

Step 1: Identify the number of Junctions.

Step 2: Assign voltage to the junctions and branch currents.

Step 3: Apply KCL at each Junction

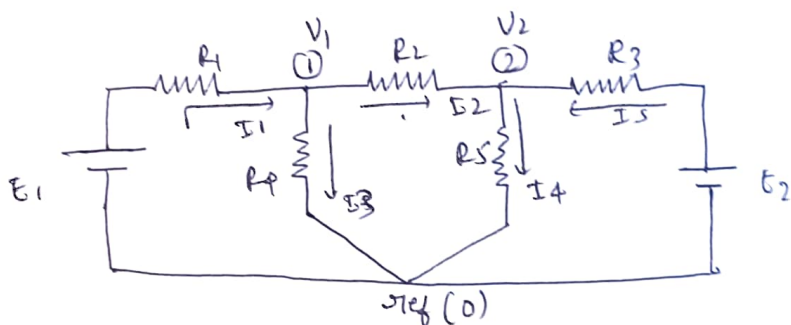

Junction 1,

$$I_1 = I_2 + I_3$$

$$\frac{E - V_1}{R_1} = \frac{V_1 - V_2}{R_2} + \frac{V_1}{R_4}$$

$$\frac{E}{R_1} = \frac{V_1}{R_1} + \frac{V_1}{R_2} - \frac{V_2}{R_2} + \frac{V_1}{R_4}$$

$$= V_1 \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4} \right] + \left(\frac{-V_2}{R_2} \right) \quad (1)$$

Junction 2.

$$I_4 = I_2 + I_5$$


$$I_5 = I_4 - I_2$$

$$\frac{E_2 - V_2}{R_3} = \frac{V_2}{R_5} - \left(\frac{V_1 - V_2}{R_2} \right)$$

$$\frac{E_2}{R_3} = \frac{V_2}{R_3} + \frac{V_2}{R_5} - \frac{V_1}{R_2} + \frac{V_2}{R_2} \rightarrow \frac{E_2}{R_3} = V_2 \left[\frac{1}{R_3} + \frac{1}{R_5} + \frac{1}{R_2} \right] + \left(\frac{-V_1}{R_2} \right)$$

$$\begin{bmatrix} \frac{E_1}{R_1} \\ \frac{E_2}{R_2} \end{bmatrix} = \begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4} & -\frac{1}{R_2} \\ -\frac{1}{R_2} & \frac{1}{R_3} + \frac{1}{R_2} + \frac{1}{R_4} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

①

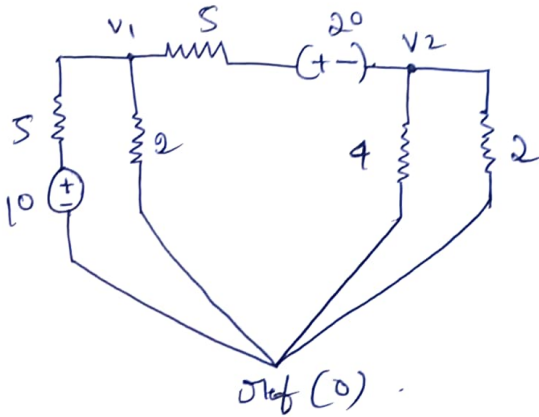

$$\begin{bmatrix} \frac{10}{5} + \frac{20}{5} \\ -\frac{20}{5} \end{bmatrix} = \begin{bmatrix} \frac{1}{5} + \frac{1}{5} + \frac{1}{2} & -\frac{1}{5} \\ -\frac{1}{5} & \frac{1}{5} + \frac{1}{2} + \frac{1}{4} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} 6 \\ -4 \end{bmatrix} = \begin{bmatrix} \frac{2}{5} + \frac{1}{2} & -\frac{1}{5} \\ -\frac{1}{5} & \frac{1}{5} + \frac{1}{2} + \frac{1}{4} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$