

2.SELECTIVITY OF TUNED CIRCUITS FREQUENCY RESPONSE

Date submitted : 03-04-2022 04:27:01

USN : 01FE21BEC268
Name : PRASHANTH SHIVAKUMAR ASKI
Department : Physics
Roll Number : 1736
Subject Name : Applied Physics Lab (ES)

Number of Observations : 19

SI No	Record of Observations	Values	Units
1	Resistance (R)	50	Ω
2	Capacitance (C)	0.1	μF
3	Inductance (L)	10	mH


Series Circuit		
SI No.	Frequency 'f' in KHz	Current 'I' in mA
1	1	4.05
2	2	7
3	3	9.6
4	3.8	10.38
5	3.9	10.4
6	4	10.42
7	4.1	10.44
8	4.2	10.45
9	4.3	10.51
10	4.4	10.5
11	4.5	10.46
12	4.6	10.43
13	4.7	10.41
14	5	10.31
15	6	9.52
16	7	8.68
17	8	7.25
18	9	7.15
19	10	6.72

Parallel Circuit		
SI No.	Frequency 'f' in KHz	Current 'I' in mA
1	1	10.94
2	2	10.08
3	3	7.93
4	3.8	4.68
5	3.9	4.28
6	4	3.98
7	4.1	3.44
8	4.2	3.25
9	4.3	3.04
10	4.4	3.16
11	4.5	3.24
12	4.6	3.69
13	4.7	3.98
14	5	4.45
15	6	7.52
16	7	9.07
17	8	9.89
18	9	10.47
19	10	10.6

2.SELECTIVITY OF TUNED CIRCUITS FREQUENCY RESPONSE

Series Circuit Graph :

Current (mA)

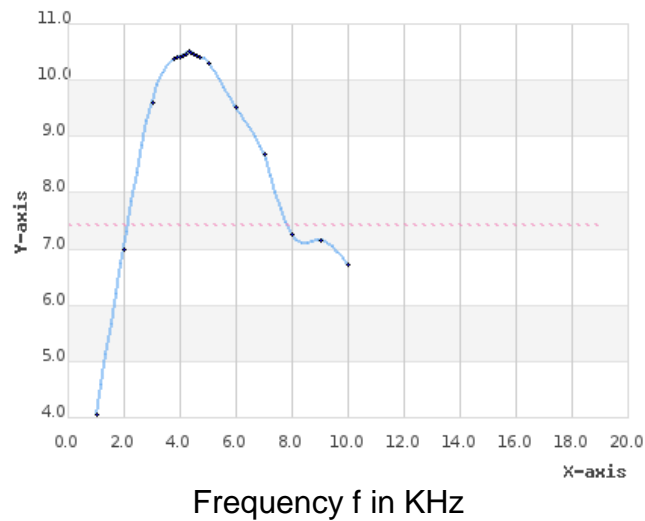


Calculation

Series resonance frequency f_r	4.3	KHz
I_{max}	10.51	mA
Band Width = $(f_b - f_a)$	1.3	Hz

Parallel Circuit Graph :

Current (mA)

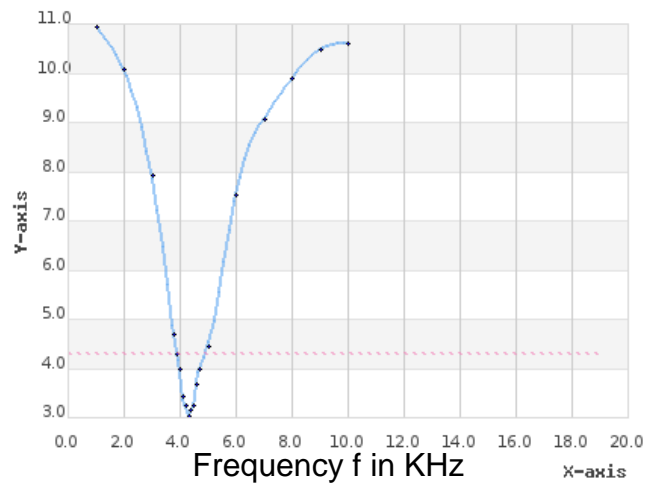

Calculation

Parallel resonance frequency f_r	4.3	KHz
I_{max}	3.04	mA
Band Width = $(f_b - f_a)$	5.7	Hz

2.SELECTIVITY OF TUNED CIRCUITS FREQUENCY RESPONSE

Tabulation

Type Of Resonance	R in Ω	L in mH	C in μF	$f_r = \frac{1}{2\pi\sqrt{LC}}$ in KHz	f_r (experimental) in KHz
Series Resonance	50	10	0.1	5.03	4.3
Parallel Resonance	50	10	0.1	5.03	4.3

Conclusion

The resonance frequency, quality factor and band width of a given LCR circuit which were connected in series and parallel were calculated experimentally and then resonance frequency was compared with the theoretically calculated value and experimentally obtained value.